

# Digital System Design with HDL (I)

## Lecture 12

Dr. Ming Xu and Dr. Kain Lu Low

Dept of Electrical & Electronic Engineering

XJTLU

# Algorithmic State Machine Design


- As an alternative to using state graphs, a **state machine flow chart** or **SM chart** may be used to describe the behaviour of a state machine.
- The ASM chart is a flowchart which resembles to the conventional software flowchart.
- The ASM chart expresses the concept of a **sequence of time intervals** in a precise way.
- The software flowchart describes only the **sequence of events** and not their duration.

# States and Clock


- The algorithmic state machine (ASM) moves through a sequence of states.
- It is the task of the **present state** of the system to:
  1. Produce any required **output signals**.
  2. To use appropriate input information to move, at the proper time, to the **next state**.
- In synchronous systems the state times are determined solely by the *master clock*.
 
# States


- Each active transition of a clock causes a change of state from the *present* state to the *next* state.
- The symbol for a state is a rectangle with its symbolic name enclosed in a small circle (or oval) at the upper left corner.
- The outputs are written inside the state box.



# Sequential ASMs

 


 - We could represent a purely sequential algorithm as an ASM chart of a sequence of states.
- The timing diagram for the above sequence of states is as follows.
- You should think of time as rigorously implied in the ASM chart notation.



 
# Branches

- We need to express conditional branches so that the next state is determined not only by the present state but also by one or more test (status) inputs.
- The symbol is the same as in conventional flowcharts for software: the diamond or diamond-sided rectangle.




## Branches –cont.

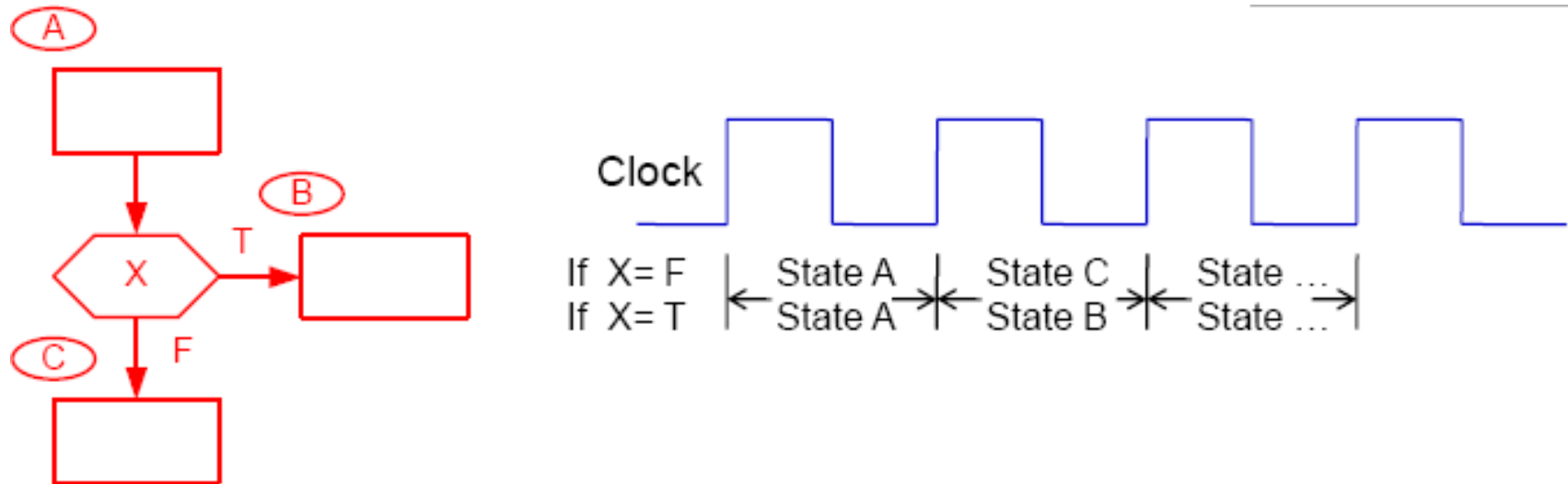

- The decision to jump to either state B or state C is made during state A and the jump occurs at the end of state A.
- The test does not require a separate clock period, it is done in parallel with the actions of the parent state rectangle and thus is part of the parent state.
 
# Multi-Way Branches


- We may draw a sequence of diamonds or have more than two paths coming from the same diamond.
- Figure (a) conveys the wrong feeling that the test of variable P is of a higher priority than the test of Q.
- For every valid combination of the input variables, there must be exactly one exit path defined.





 
# Outputs

- To indicate an output, a command description is placed within the appropriate state rectangle.
- The first line, MOVING, calls for the assertion of the signal MOVING, during the state i.e. MOVING = TRUE.
- The last line means that the output STATUS is to have the value of the variable ERRFLAG(Tor F) during this state.


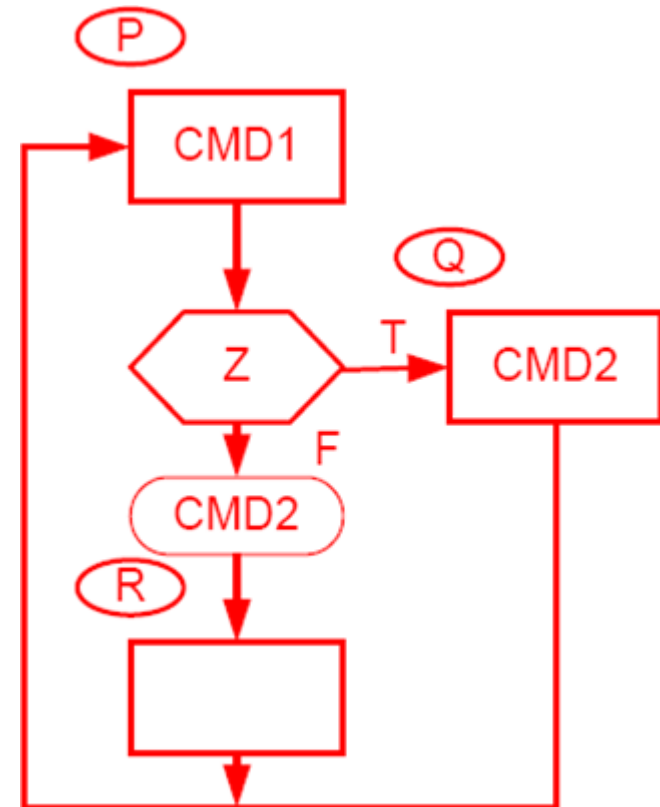
# Conditional Outputs

- Sometimes we want a command to occur only when some other condition exists.
- We call such a command a **conditional output** and specify it with an oval.
- CMD2 will occur for one state time whenever the ASM is in state Q. When in state P, CMD2 will occur if test input Z is false.
- CMD2 is an unconditional output in state Q and a conditional output in state P.




# Summary of ASM Symbols

- Test inputs may serve two functions in ASM charts:
  - They may help specify the next state
  - They may control the issuing of conditional outputs.
- Ovals for conditional outputs and diamonds for test inputs belong to the parent state; since the activities occur **concurrently** during the state time.
- A state thus consists of its rectangle, which is always present, and any test diamonds and conditional output ovals associated with that state.
- Unconditional outputs are a function only of the parent state. Conditional outputs depend on both the state and the path within the state.

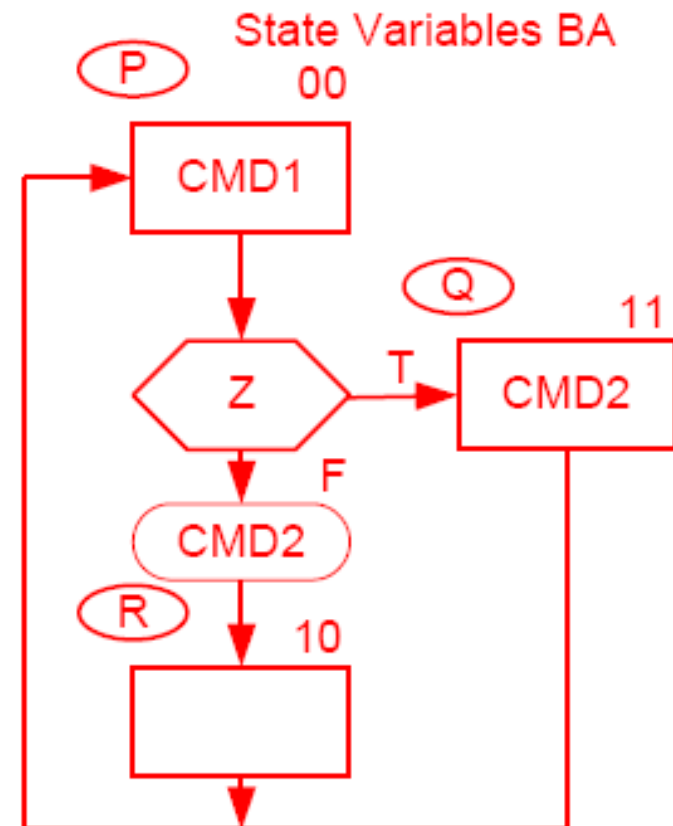
# Traditional Design Implementation

- Use flip-flops as state memory (either D, T, or J-K types)
- There are two ways to represent the present state in flip-flop memory
  - Assign a unique binary number to each state (**Encoding Method**).
  - Assign one flip-flop to each state (**One Hot Method**).
- Using the **Encoding method**, two state variables are required for encoding 3 states.
- The state assignment is arbitrary.



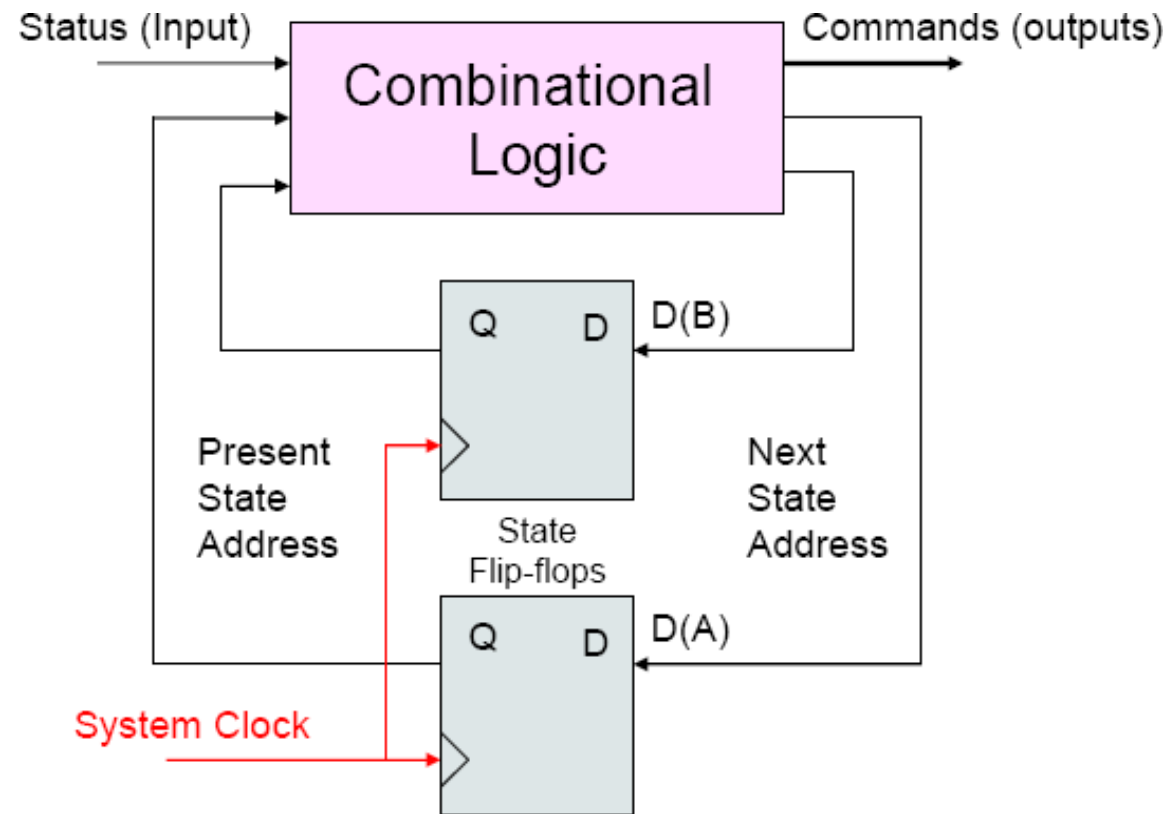
# Process Model

Given the present state we need to compute the new state code to load into the state flip flops.



# State Transition Table

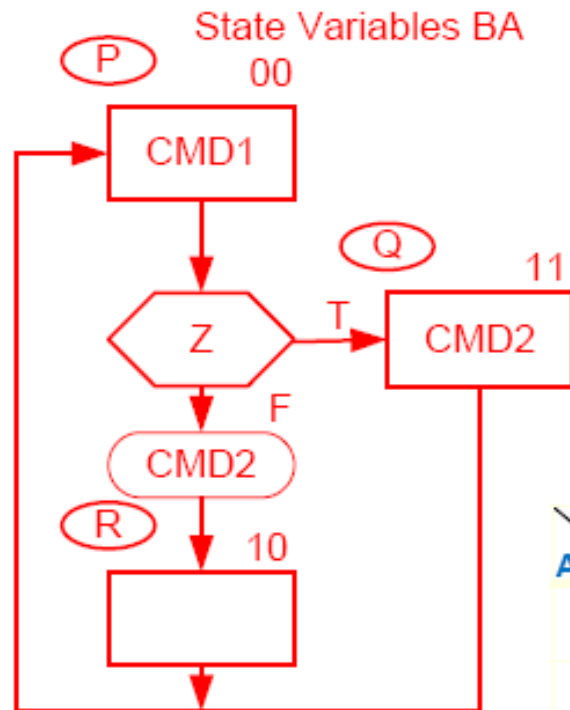

Present State	Input	Next State	Outputs	
AB	Z	D(A)D(B)	CMD1	CMD2
00	0	10	1	1
00	1	11	1	0
11	-	00	0	1
10	-	00	0	0
01	-	-	-	-

AB \ Z	Z	
	0	1
00	1	1
01	X	X
11	0	0
10	0	0

AB \ Z	Z	
	0	1
00	0	1
01	X	X
11	0	0
10	0	0

AB \ Z	Z	
	0	1
00	1	0
01	X	X
11	1	1
10	0	0

Oct. 2008


$$\text{CMD1} = A'$$

$$D(A) = A'$$


$$D(B) = A'Z$$

$$\text{CMD2} = B + A'Z'$$

# ASM Implementation

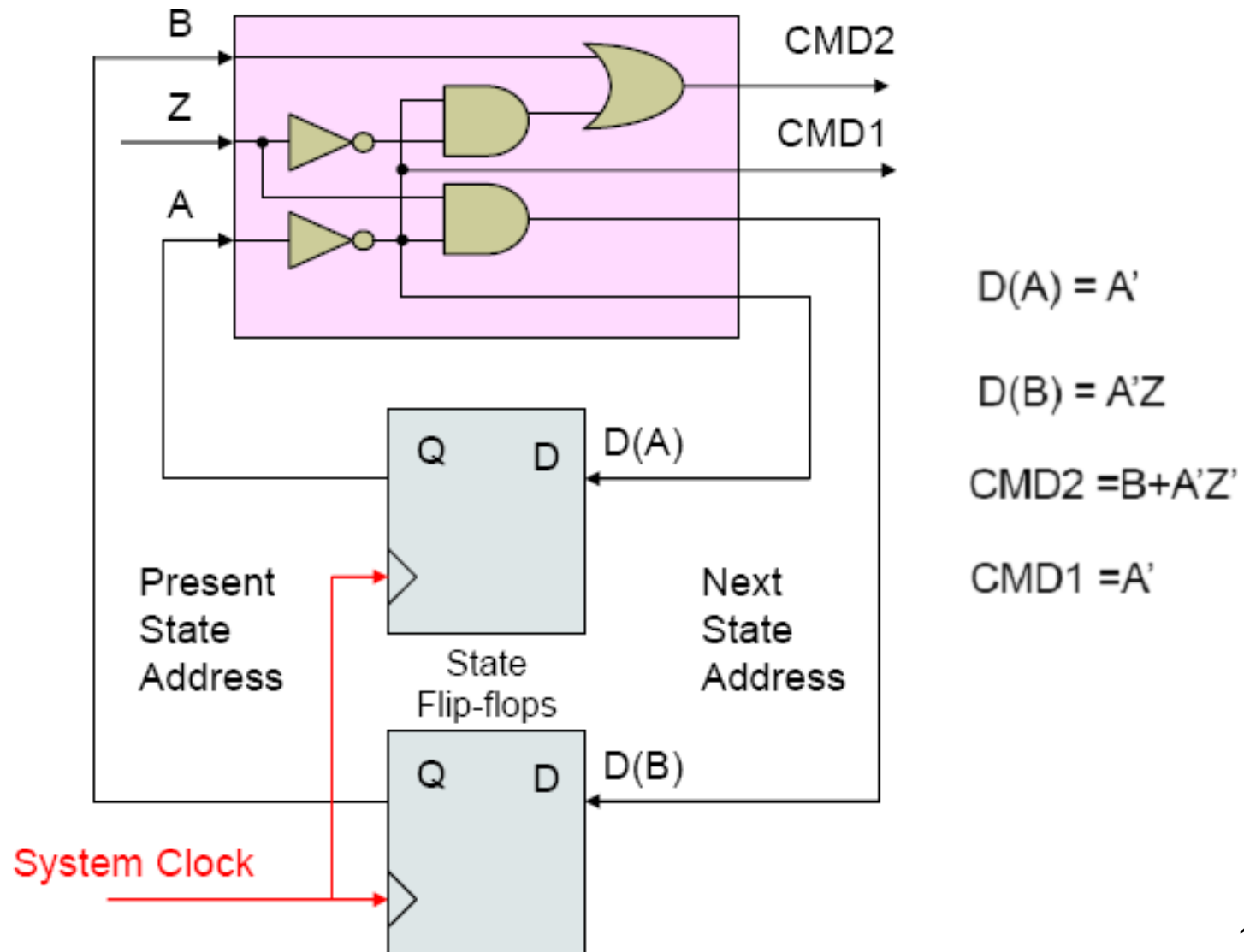

# Verilog Code

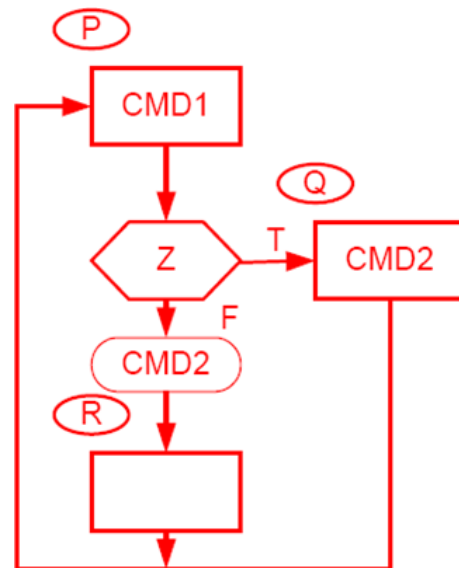

```

1
2 module ASM1(Z, CMD1, CMD2, clk, reset);
3     output    CMD1, CMD2;
4     input     Z , reset , clk ;
5
6     parameter P = 2'b00;
7     parameter Q = 2'b11;
8     parameter R = 2'b10;
9
10    reg [1:0]  state, next_state;
11    reg        CMD1, CMD2;
12
13    always@ (posedge clk)
14        if (reset == 0) state <=P;
15        else state <=next_state;

```

```

17 always @ (state or Z) begin
18     CMD1 = 0; CMD2 = 0;
19     case (state)
20     P: begin
21         CMD1 = 1;
22         if(Z == 1) next_state = Q;
23         else begin
24             next_state = R;
25             CMD2=1; end
26         end
27     Q: begin
28         CMD2=1; next_state = P;
29         end
30     R: next_state = P;
31     default : next_state = P;
32     endcase
33 end
34 endmodule

```