 


Topic 4: Building memory

Flip-flop 触发器

Register(寄存器) and Counter(计数器)

Setting an S-R flip-flop



S=1, R=0, Q=0 复位

Q_0	S	R	Q
0	1	1	0
1	1	1	1
0	0	1	1
1	0	1	1
0	1	0	0
1	1	0	0

2

A simple sequential logic

S-R flip-flop (触发器)

- This “remembers” one of 2 possible *states*
 - Two outputs Q and Q' and feedback is introduced
 - Q_n is the ‘present’ **state**; Q_{n+1} is the ‘next’ **state(状态)**
 - Q_n means without input, Q_{n+1} means with inputs
- Q depends on the S and R inputs:
 - A low pulse on **S** always make the $Q=1$ state (set)
 - A low pulse on **R** always make the $Q=0$ state (reset)
 - When S or R returns to high after the low pulse, **Q stays where it is**
 - and so the flip-flop “remembers” if it is in state $Q=1$ or state $Q=0$
 - We’re “not allowed” to have S and R both low simultaneously

Combinational logic and sequential logic 组合逻辑 时序逻辑


- The defining feature of combinatorial logic is that its outputs are **purely a function of its inputs** (ALU, voter, flags.....)
- The defining feature of sequential logic is that its outputs are a **function of its inputs and of its current outputs(Register)**
 - This involves **feedback(反馈)** of the outputs to the inputs
 - This feedback is the hook on which we hang memory

RS flip-flop

- Feedback is introduced
- Output Q_{n+1} is related to original Q_n
- R,S can set or reset output
- R,S=1, the output remain (keep unchanged)
- It means this bit is reserved
- Basic logic gate for sequential circuit
- $Q_{n+1} = S' + QR$: state equation

Limitations of the S-R flip-flop

- There are two problems in using an S-R flip-flop to implement a bit in a register
 1. It has distinct SET and RESET inputs
 - We'd ideally like just a **single input** that "sets" the state if it's 1 and "resets" the state if it's 0
 2. We have no way of telling the flip-flop exactly **when** it should store input data
 - We'd like a "**latch**" signal for this to work in a practical system under the supervision of a **control unit**

 




D-type flip-flop

RS→D 触发器

 - Add a latch as control to two gates
- D is input data
- Add a NAND Gates



Latch?
锁存




D-type latch

D锁存器

Q_0	D	L	Q
0	0	0	
1	0	0	
0	0	1	
1	0	1	
0	1	0	
1	1	0	
0	1	1	
1	1	1	

} "latch"
a 0

} "latch"
a 1

 

Latch?
锁存



Latching in a 1


L=1, RS flip-flop
L=0 reserved

Truth table

Q_n	D	L	Q_{n+1}
0	0	0	0
1	0	0	1
0	0	1	0
1	0	1	0
0	1	1	1
1	1	1	1

} "latch"
a 0


} "latch"
a 1

 

Difference from RS flip flop


- One input $Q_{(n+1)}=D$ $L=1, Q=D$
- One control $Q=Q_0$ $L=0$: keep D
- Latch one bit
- Hold the one bit in latch high

D latch symbol

 


$L=1$ Latch is open
 $L=0$ Latch is closed
 D flip flop is one bit register
 D flip flop is the basic unit for register

D flip flop D触发器

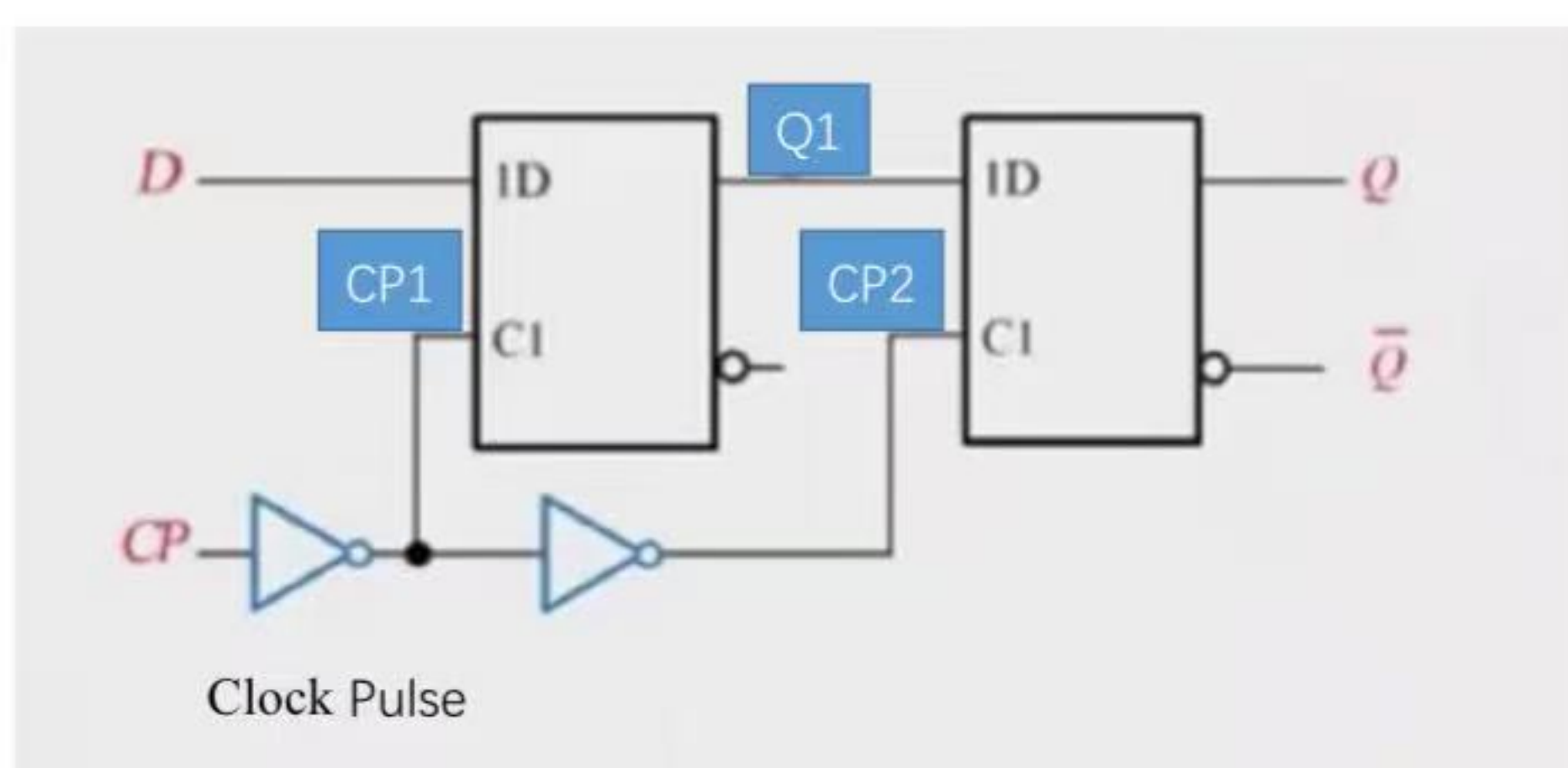


In what case, $Q=D$?
 Benefit?

Master latch Slave latch


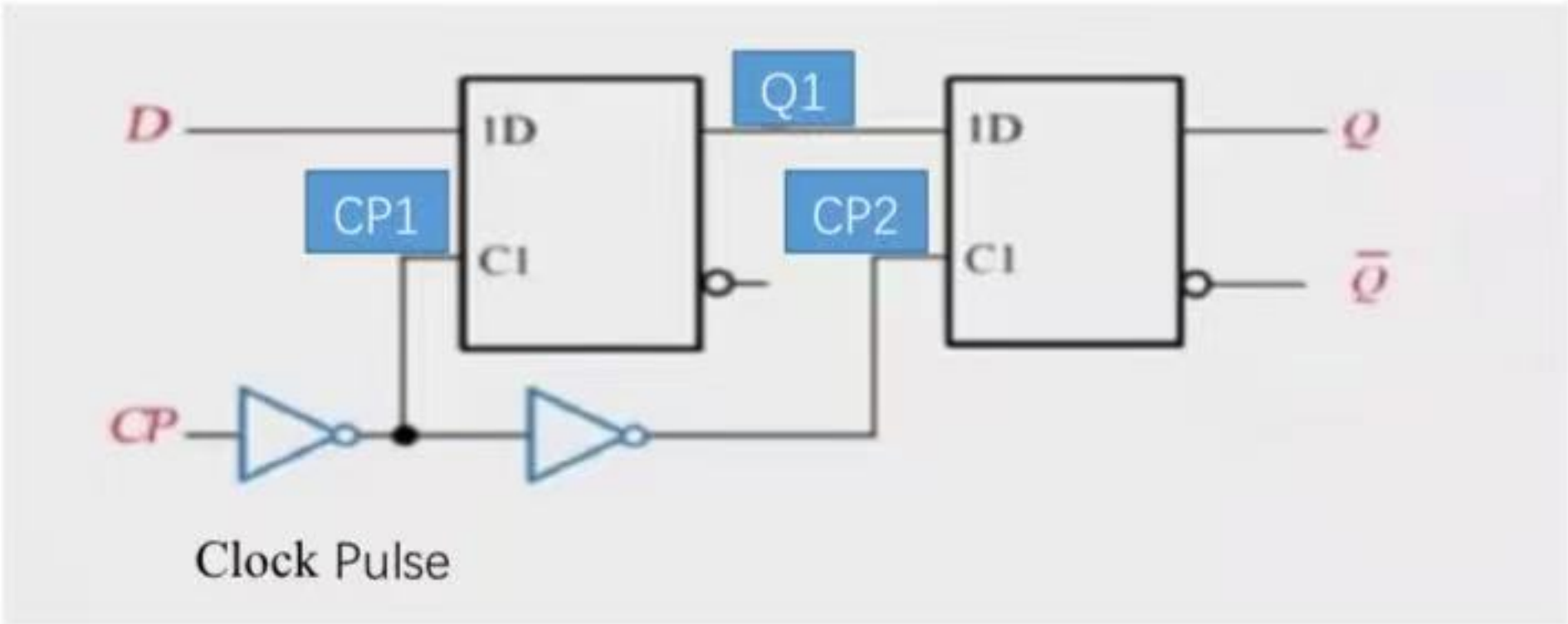


Waveform 波形
Draw Q1, Q

 CP control to store
下降沿触发，脉冲触发
在瞬间触发，降低干扰



Waveform 波形
Draw Q1, Q

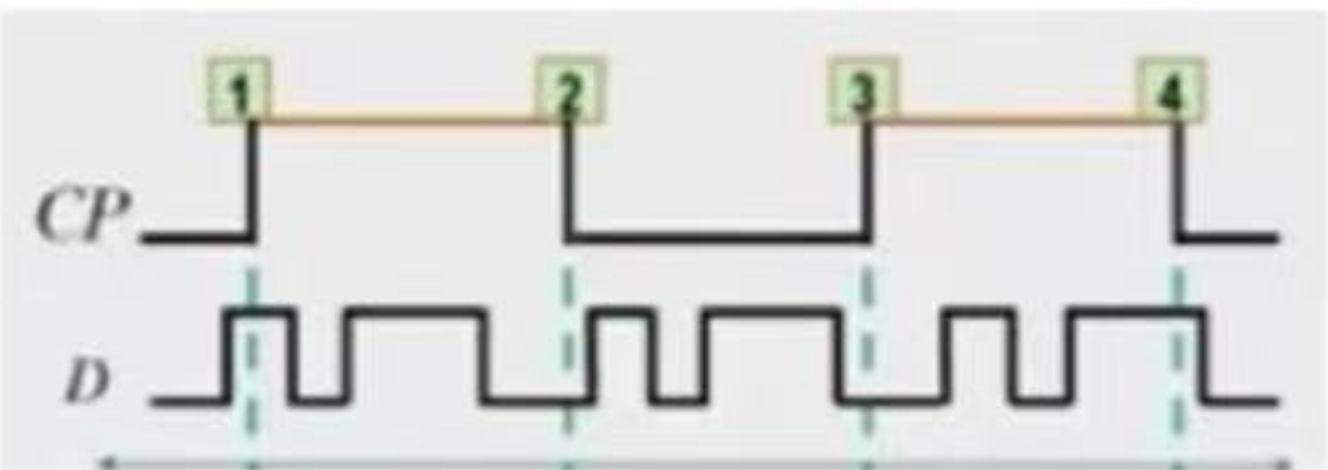 

D0 is effective input
D1 ,D2 D3 are interference
D4 is effective input
Only D1 and D4 are reserved


Compare Q1, Q,
Q1: interference
Q: No interference
In CP edge, Q=D

CP control to store




CP=0, 外部信号进入Q1, Q不变
CP=1, Q1进入Q输出, 外部信号不进入, D1,D2,D3抑制


Assume: interference

 

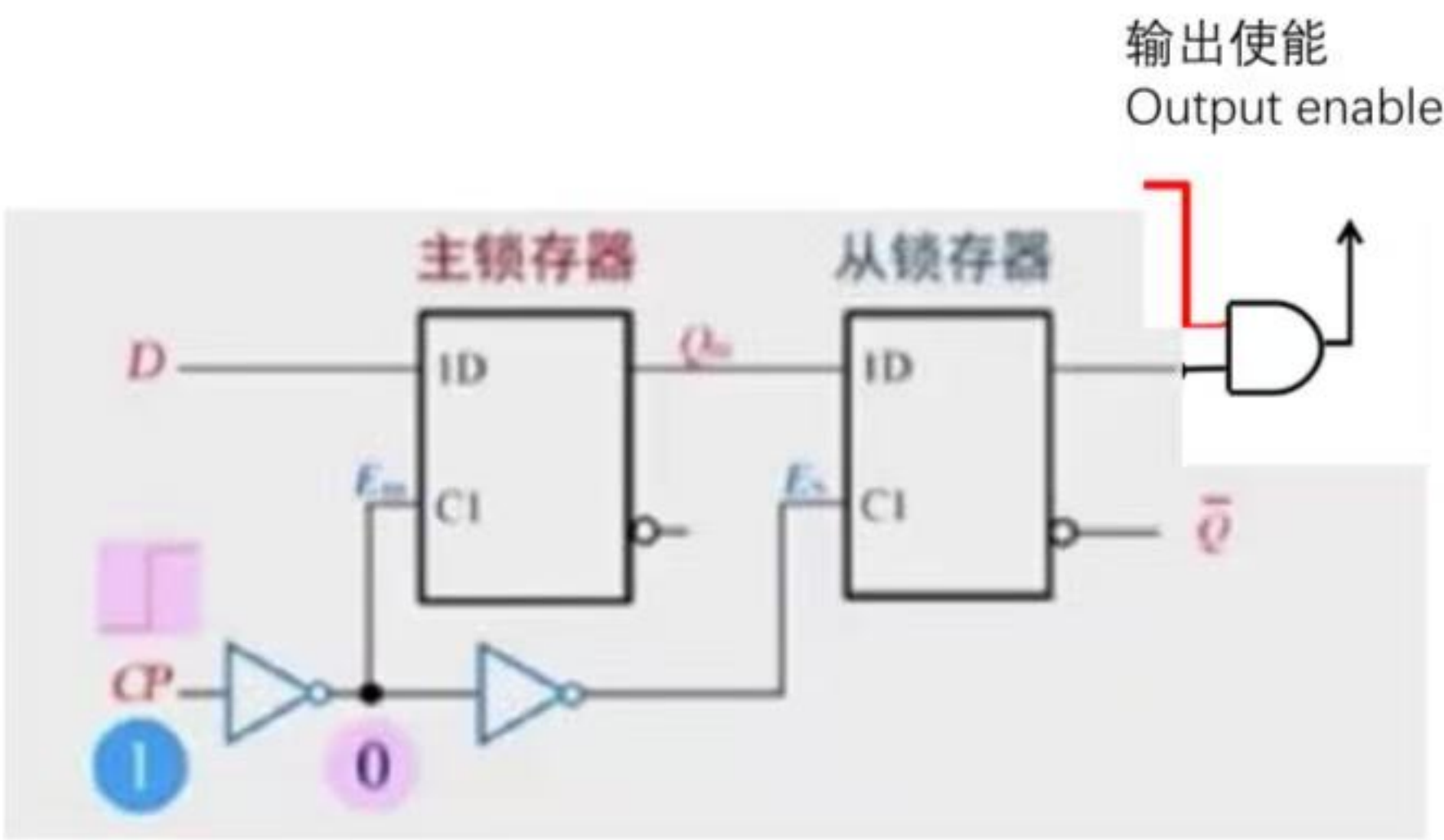CP rising edge triggering
CP=0, Q1=D, Q remain; CP=1, Q1 remain, Q=D and remain
Q =D at rising edge
Advantage: anti-interference




D flip flop

 


Rising edge trigger

Waveform for edge triggering D flip-flop

 


Draw Q_{n+1}
What tools are used?

JK flip-flop

 


CP=1, J=K=0,	Q remain	Q' remain
CP=1, J=0, K=1	Q=0,	Q'=1
CP=1, J=1, K=0	Q=1,	Q'=0
CP=1, J=1, K=1	Q'	Q

JK flip-flop

 


CP=1, J=K=0,	Q	Q'
CP=1, J=0, K=1	Q	Q'
CP=1, J=1, K=0	Q	Q'
CP=1, J=1, K=1	Q	Q'

T flip-flop

 

T	Q_{n+1}
0	Q_n
1	$\sim Q_n$

Where is CP from?

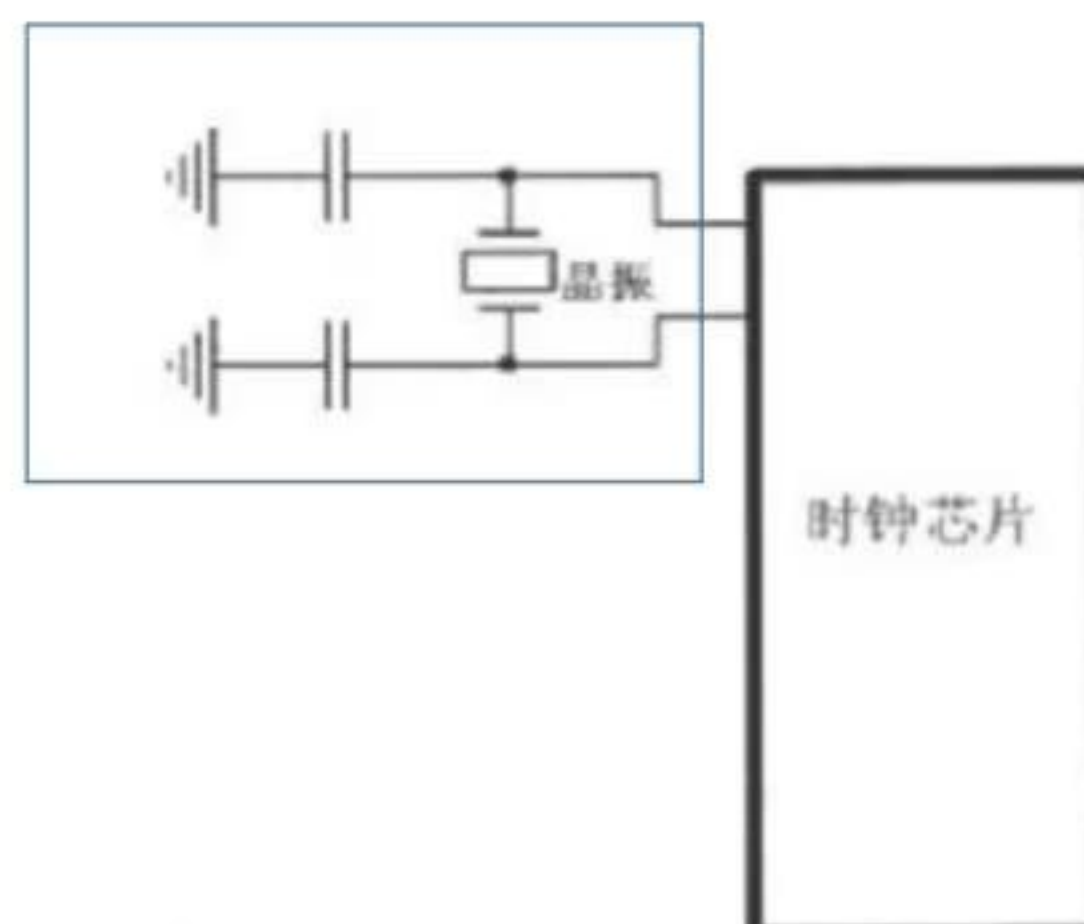


Clock pulse circuit

Where is CP to?

- CP is control signal
- CP is input to control unit of each computer components, such as CPU CU, memory CU, other controller.
- CU is the core of CPU


How to build register?

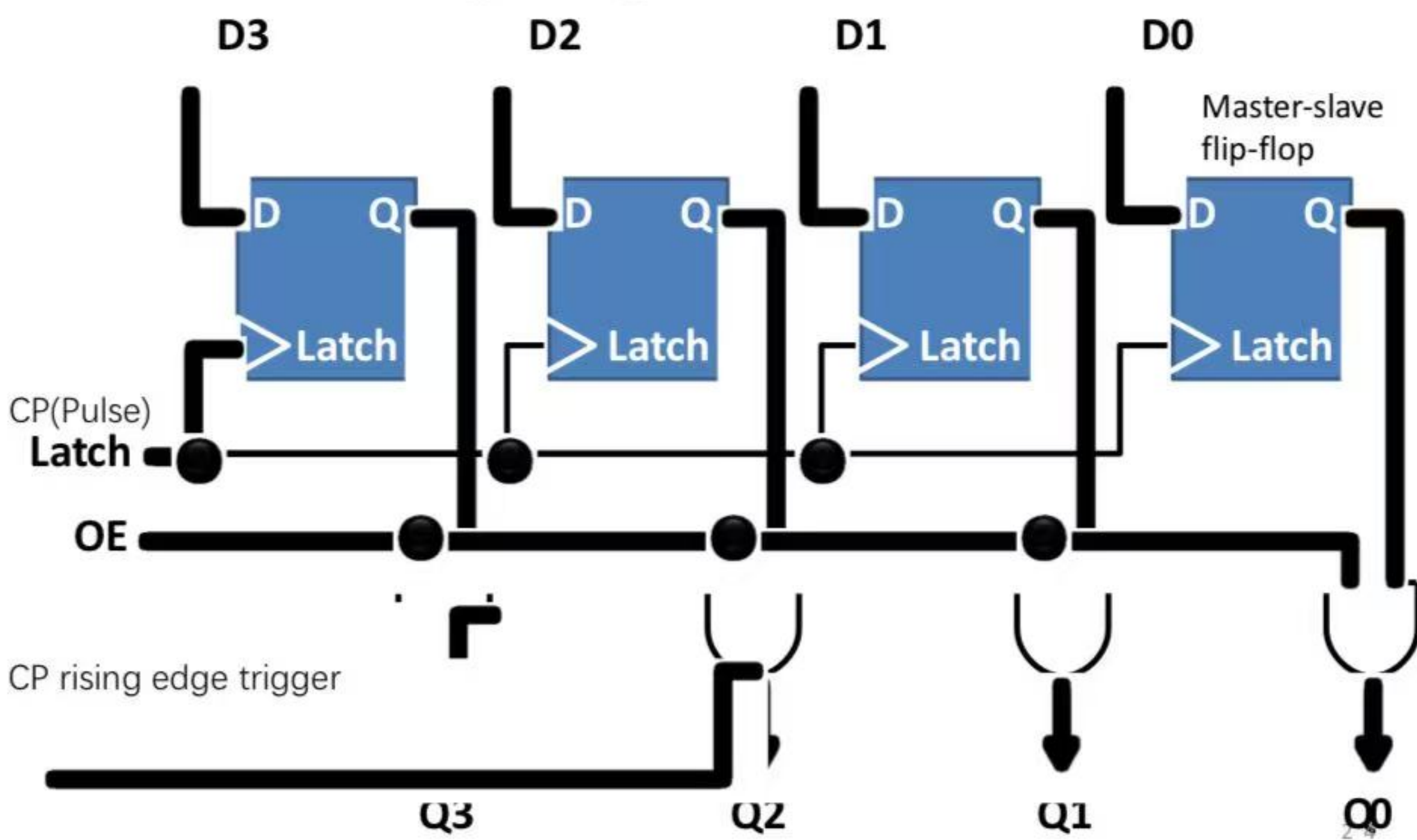Implementing a register using multiple flip-flops



Draw the sequential diagram
Analyze the logic gate function

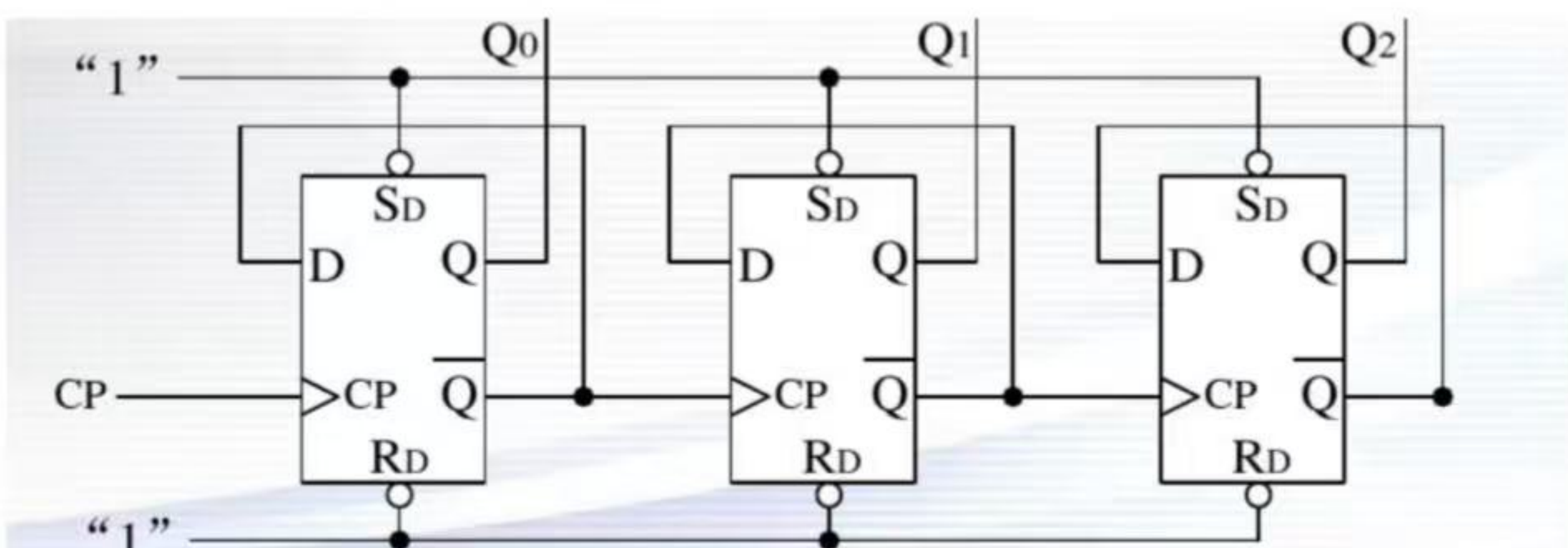
(S is set control, R is reset control, assume $Q_0=0$, $Q'_0=1$)
(low level is effective)




Write logic status equation

Draw sequential waveform



 


Assume $Q_{0,1,2}=0, Q'_{0,1,2}=1$

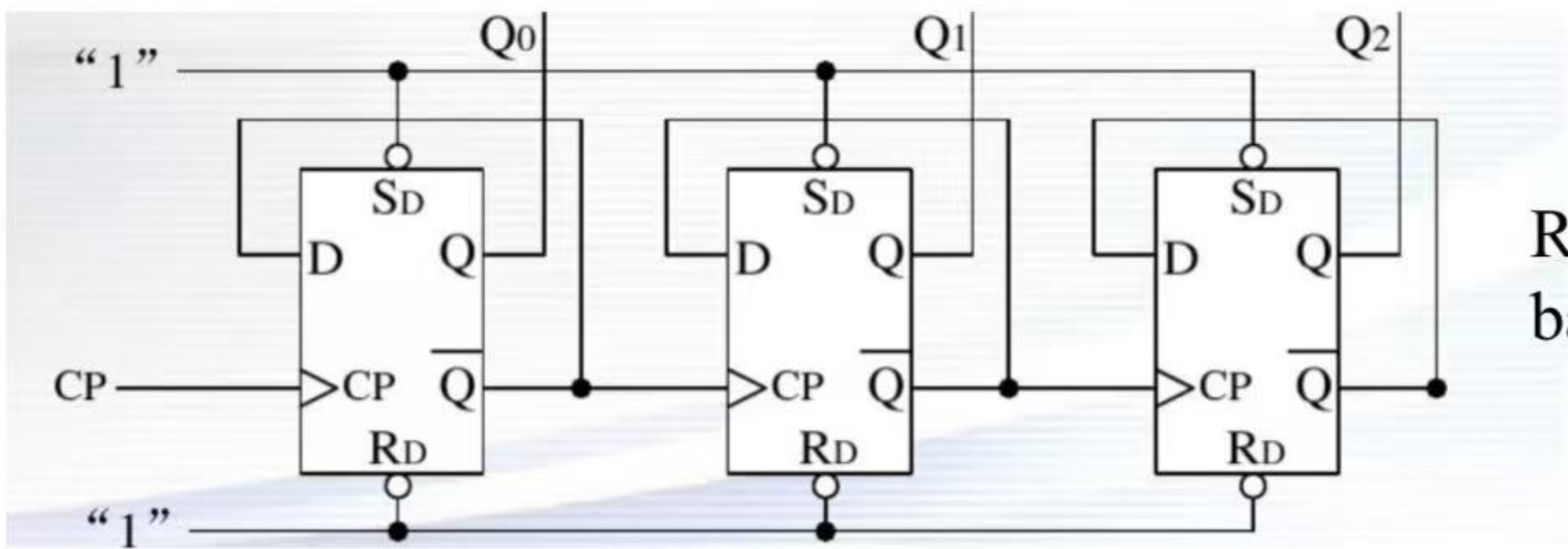


$$Q_{n+1} = D = Q'_n$$

When CP ascending is coming

 


Base?

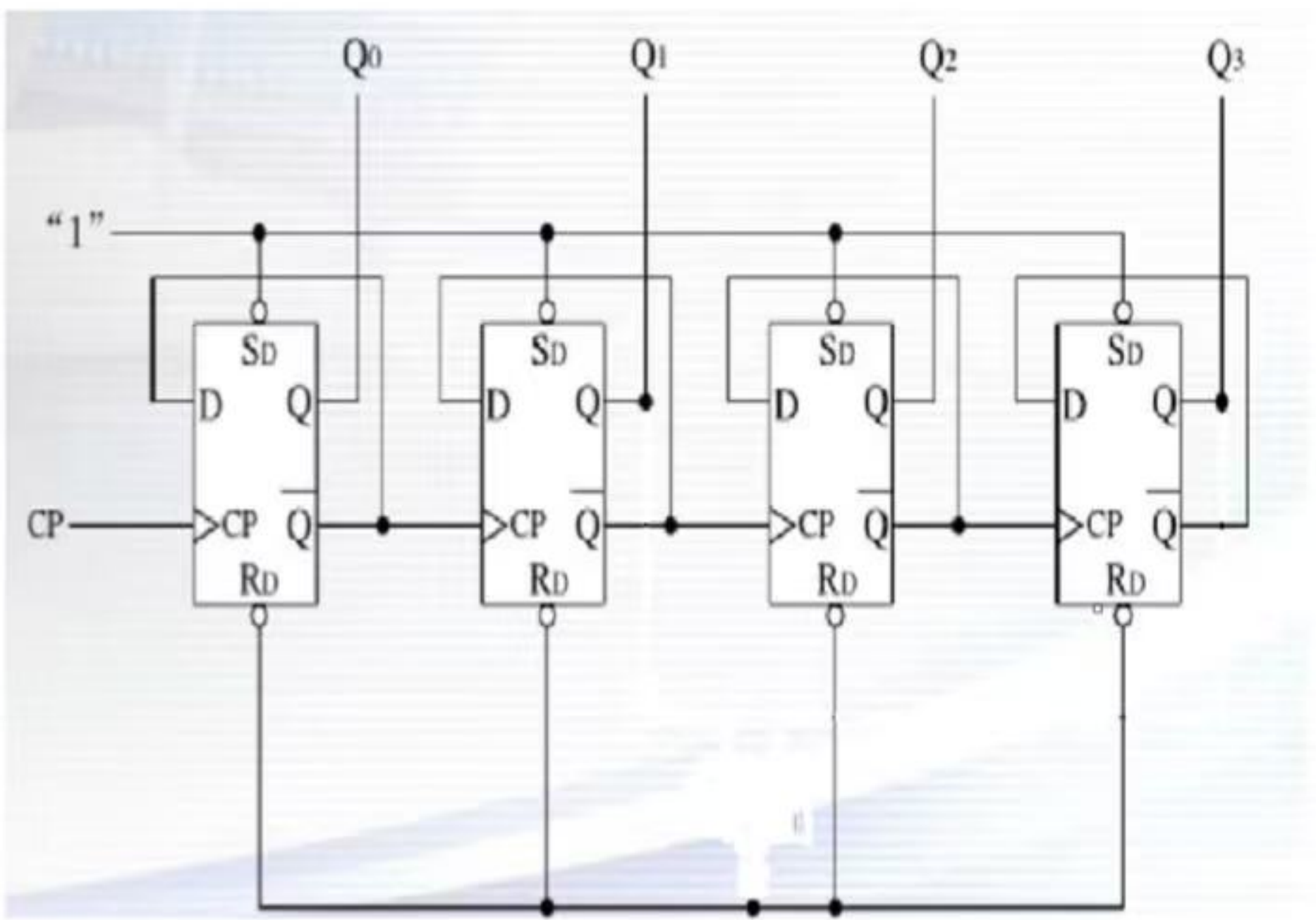


Draw the sequential diagram
Analyze the logic gate function

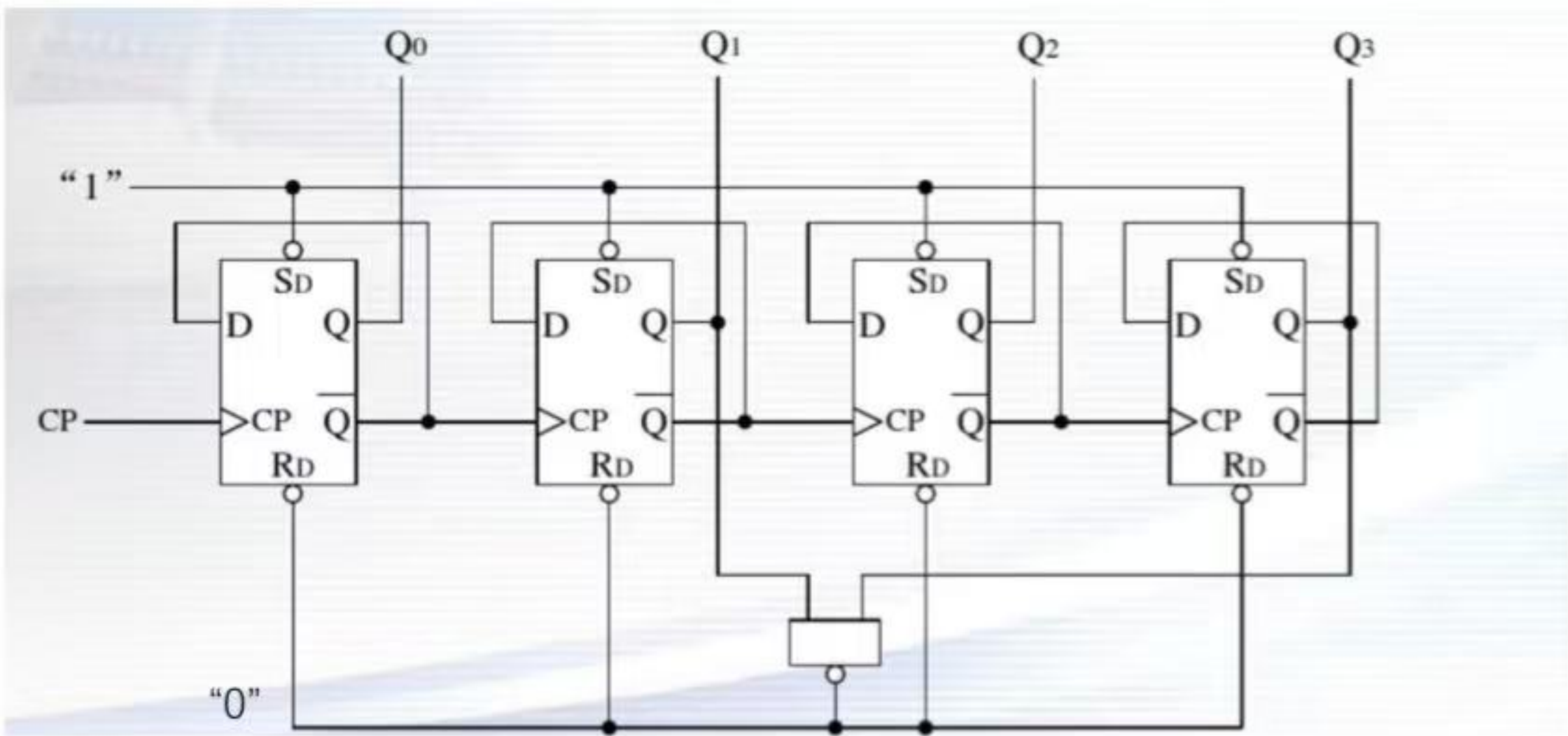
(S is set control, R is reset control, assume $Q_0=0$)



Counter
(Timer)

Frequency divider, (分频器)

 

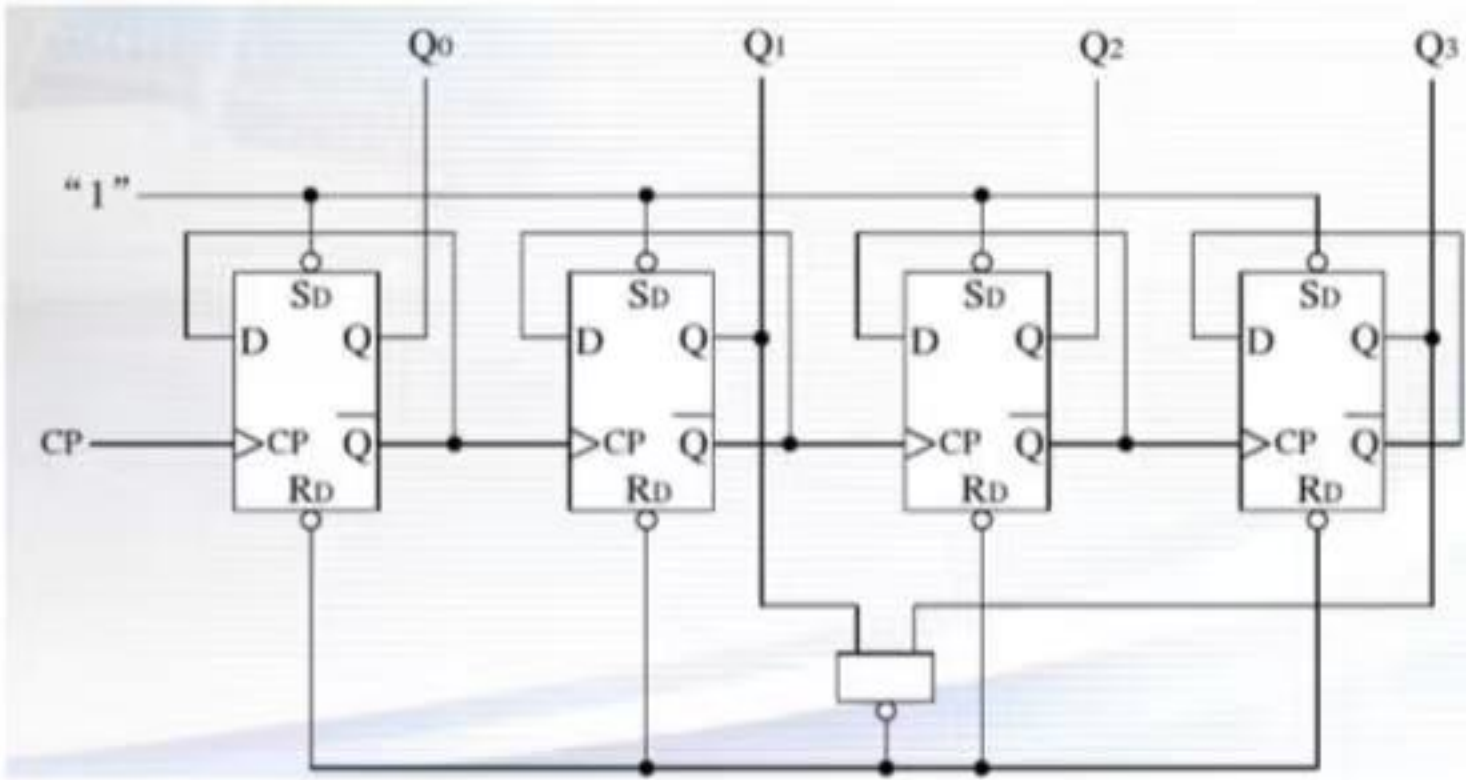

Frequency divider
(分频器)


Generate different frequency signal

Used for different CU control

Counter
(计数器)

Cp1: Q0=1
Cp2: Q1=1
Cp3: 11
Cp4: Carry out
Frequency meter

Shift right register

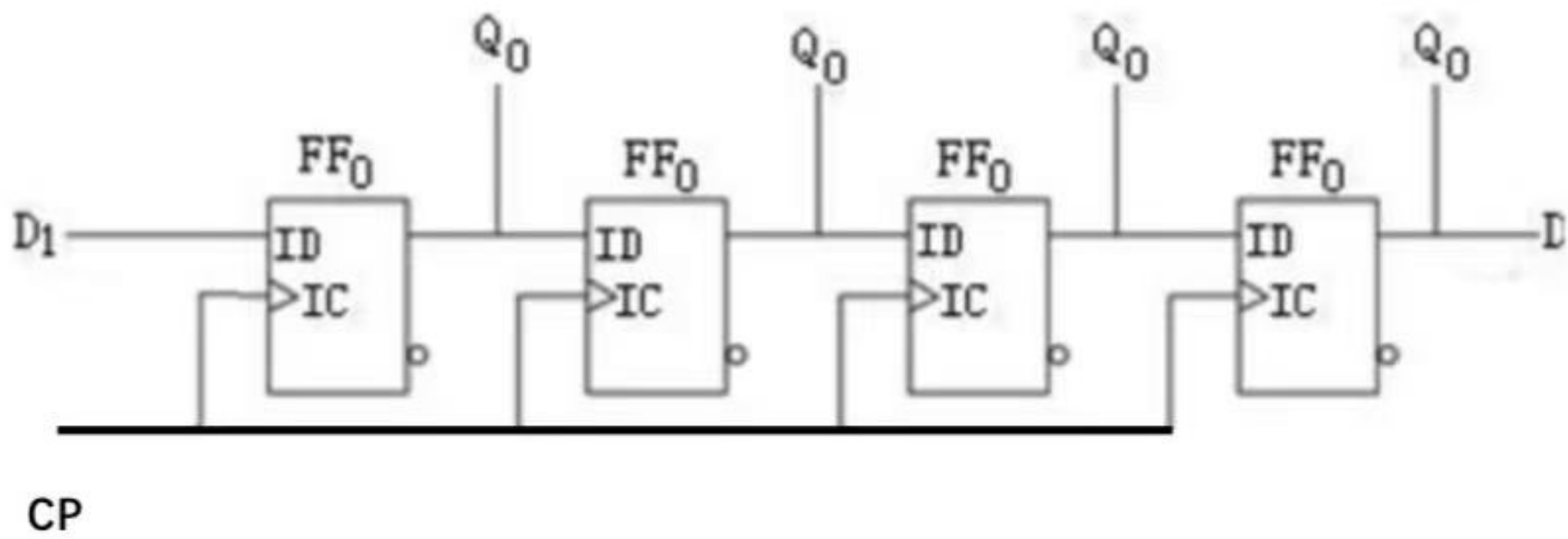


CP

Serial input D1 and parallel out

shifting right

synchronous trigger

Loop shift register

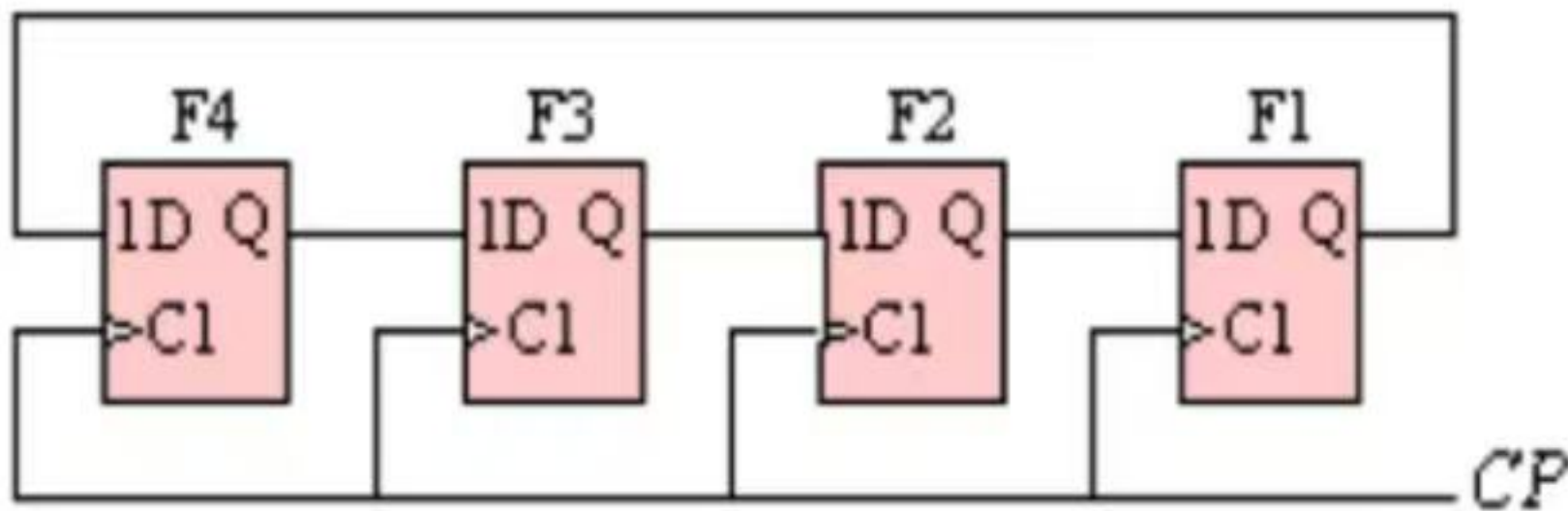

Loop

Initial state: F4F3F2F1:1000

	F4	F3	F2	F1
0	1	0	0	0
1	0	1	0	0
2	0	0	1	0
3	0	0	0	1
4	1	0	0	0

Buses: connecting the blocks


- Buses are the “glue” of the computer architecture
 - They connect the elements of the von Neumann architecture: the ALU, the control unit, memory chips, and I/O devices
 - They are essentially bundles of wires, one for each bit
- There are three types of bus
 - An *address bus* runs between the control unit and main memory
 - Used to tell main memory to access a specific address (whether for reading or writing)
 - The “width” of the address bus corresponds to the amount of addressable memory
 - Examples: 16 bits \rightarrow 65536 bytes (2^{16}); 32 bits \rightarrow 4 GB (2^{32})
 - Data buses carry data around the computer
 - An “n-bit” processor will have a data bus n bits wide (e.g. $n=8$ or 32 or 64)
 - This means we can read/ write n bits from/ to memory in one go
 - Some processors have distinct internal and external data buses
 - External bus may be narrower to reduce the number of external connections/ pins, and thus cost
 - Control bus

25

Data buses: connecting to registers

Explanation

- Bus wires are *shared*

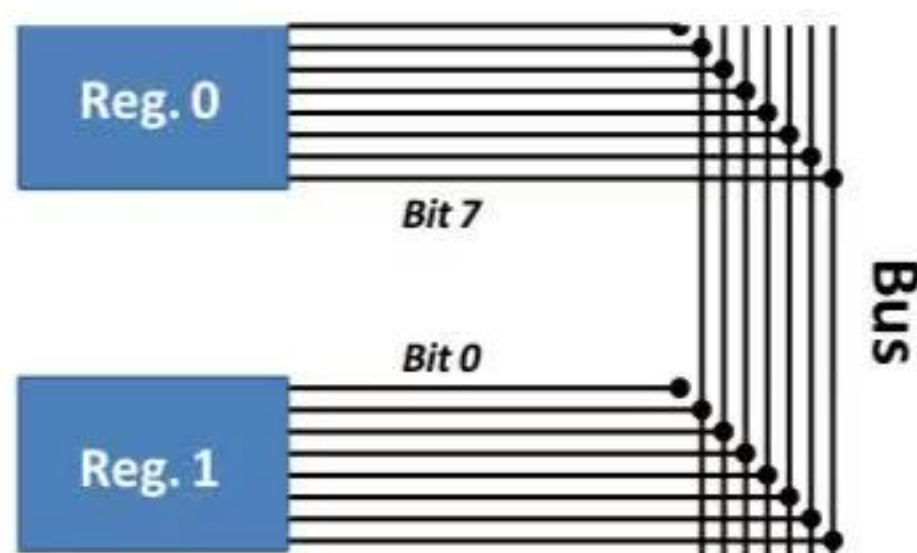

... so we must ensure that there is only one active output at a given time?

A job for **output enable**...

Summary

- We know the difference between **combinatorial and sequential logic**
- We know how logic components can be used to **build one bit of static storage** (static memory) **flip flop**
we know how these bits can then be combined into multi-bit **Registers and counter**
- We understand how the elements of the computer architecture can be glued together using **buses**

29

Exercise

1: Draw out the D flip-flop symbol, explain the meaning of CP, D, Sd, Rd, Q, Enable.

2: Draw base-6 counter logic circuit

Draw the waveform of base_6 counter

3. Design any number system counter(任意进制, 如54进制, 前50个10进制, 后4个位5进制)

Exercise after class

- Design 60 base counter
- Design a timer(counter based on subtraction)