

Digital System Design with HDL (I)

Lecture 7

Dr. Ming Xu and Dr. Kain Lu Low

Dept of Electrical & Electronic Engineering

XJTLU

In This Session

- Functions and Tasks
- Verilog for Combinational Circuits
 - Multiplexers
 - Decoders
 - Encoders
 - Comparators

Functions

- A function is a part of the code that may be re-used and thus separated from the other parts in a module.

- Syntax:

function [*size_or_type*] function_name;

input declarations

local variable declarations

procedural statements

endfunction


size_or_type (optional) is the returned type or range as [*msb:lsb*]. The default is a 1-bit value.

Functions

- Functions should have at least one input.
- The function name serves as the *only* output variable. No other output or inout is allowed.
- Functions are only defined within a module.

Functions

Example: a 16-to-1 multiplexer

 

```
module mux_f (W, S16, f);
```

```
  input [0:15] W;
```

```
  input [3:0] S16;
```

```
  output reg f;
```

```
  reg [0:3] M;
```

```
  function mux4to1;
```

```
    input [0:3] W;
```

```
    input [1:0] S;
```

```
    if (S == 0) mux4to1 = W[0];
```

```
    else if (S == 1) mux4to1 = W[1];
```

```
    else if (S == 2) mux4to1 = W[2];
```

```
    else if (S == 3) mux4to1 = W[3];
```

```
  endfunction
```

```
  always @(W, S16)
```

```
  begin
```

```
    M[0] = mux4to1(W[0:3], S16[1:0]);
```

```
    M[1] = mux4to1(W[4:7], S16[1:0]);
```

```
    M[2] = mux4to1(W[8:11], S16[1:0]);
```

```
    M[3] = mux4to1(W[12:15], S16[1:0]);
```

```
    f = mux4to1(M[0:3], S16[3:2]);
```

```
  end
```

```
endmodule
```

Tasks

- A task is a part of the code that may be re-used and thus separated from the other parts in a module.
- A task may have any number of inputs, outputs or inouts.
- A task does not return any value by its name.
- A task is like a subroutine.


Tasks

Syntax:

```
task task_name;  
    input declarations  
    output declarations  
    local variable declarations  
    procedural statements  
endtask
```

Tasks

Example: a 16-to-1 multiplexer

 

```

module mux_t (W, S16, f);
  input [0:15] W;
  input [3:0] S16;
  output reg f;
  reg [0:3] M;


  task mux4to1;
    input [0:3] W;
    input [1:0] S;
    output Result;
    begin
      if (S == 0) Result = W[0];
      else if (S == 1) Result = W[1];
      else if (S == 2) Result = W[2];
      else if (S == 3) Result = W[3];
    end
  endtask

  always @(W, S16)
  begin
    mux4to1(W[0:3], S16[1:0], M[0]);
    mux4to1(W[4:7], S16[1:0], M[1]);
    mux4to1(W[8:11], S16[1:0], M[2]);
    mux4to1(W[12:15], S16[1:0], M[3]);
    mux4to1(M[0:3], S16[3:2], f);
  end

endmodule

```



Combinational circuits

  

- Outputs only depend on inputs
- Could include: gates, multiplexers, encoders, decoders, code converters, comparators ...
- Verilog description: gates, logic expression, behaviour

Multiplexers

Using conditional operators



<i>s</i>	<i>f</i>
0	<i>w</i> ₀
1	<i>w</i> ₁

```
module mux2to1 (w0, w1, s, f);  
  input w0, w1, s;  
  output f;  
  
  assign f = s ? w1 : w0;  
  
endmodule
```


```
module mux2to1 (w0, w1, s, f);  
  input w0, w1, s;  
  output f;  
  reg f;  
  
  always @(w0 or w1 or s)  
    f = s ? w1 : w0;  
  
endmodule
```

Conditional operator
in continuous assignment

Conditional operator
in procedural statement

Multiplexers

Using nesting conditional operators

 

s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

```
module mux4to1 (w0, w1, w2, w3, S, f);  
  input w0, w1, w2, w3;  
  input [1:0] S;  
  output f;  
  
  assign f = S[1] ? (S[0] ? w3 : w2) : (S[0] ? w1 : w0);  
  
endmodule
```

Multiplexers


Using If-else statements

```
module mux2to1 (w0, w1, s, f);  
  input w0, w1, s;  
  output f;  
  reg f;  
  
  always @(w0 or w1 or s)  
    if (s == 0)  
      f = w0;  
    else  
      f = w1;  
  
endmodule
```

Using case statements

```
module mux4to1 (W, S, f);  
  input [0:3] W;  
  input [1:0] S;  
  output f;  
  reg f;  
  
  always @(W or S)  
    case (S)  
      0: f = W[0];  
      1: f = W[1];  
      2: f = W[2];  
      3: f = W[3];  
    endcase  
  
endmodule
```

Multiplexers

 

Hierarchical 16-to-1 Multiplexer


```
module mux16to1 (W, S16, f);
  input [0:15] W;
  input [3:0] S16;
  output f;
  wire [0:3] M;

  mux4to1 Mux1 (W[0:3], S16[1:0], M[0]);
  mux4to1 Mux2 (W[4:7], S16[1:0], M[1]);
  mux4to1 Mux3 (W[8:11], S16[1:0], M[2]);
  mux4to1 Mux4 (W[12:15], S16[1:0], M[3]);
  mux4to1 Mux5 (M[0:3], S16[3:2], f);

endmodule
```

Decoders

Decoder using case

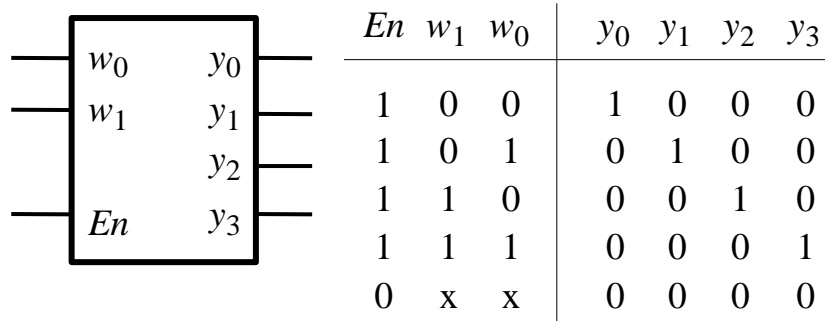

Concatenate operator

Default for $En=0$

```

module dec2to4 (W, Y, En);
    input [1:0] W;
    input En;
    output [0:3] Y;
    reg [0:3] Y;

    always @(W or En)
        case ({En, W})
            3'b100: Y = 4'b1000;
            3'b101: Y = 4'b0100;
            3'b110: Y = 4'b0010;
            3'b111: Y = 4'b0001;
            default: Y = 4'b0000;
        endcase

endmodule
    
```

Decoders

Decoder using if-else, case

<i>En</i>	<i>w</i> ₁	<i>w</i> ₀	<i>y</i> ₀	<i>y</i> ₁	<i>y</i> ₂	<i>y</i> ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

```
module dec2to4 (W, Y, En);  
    input [1:0] W;  
    input En;  
    output [0:3] Y;  
    reg [0:3] Y;  
  
    always @(W or En)  
    begin  
        if (En == 0)  
            Y = 4'b0000;  
        else  
            case (W)  
                0: Y = 4'b1000;  
                1: Y = 4'b0100;  
                2: Y = 4'b0010;  
                3: Y = 4'b0001;  
            endcase  
        end  
    end  
endmodule
```

Decoders

Decoder using for loops

<i>En</i>	<i>w</i> ₁	<i>w</i> ₀	<i>y</i> ₀	<i>y</i> ₁	<i>y</i> ₂	<i>y</i> ₃
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1
0	x	x	0	0	0	0

```

module dec2to4 (W, Y, En);
    input [1:0] W;
    input En;
    output reg [0:3] Y;
    integer k;


    always @(W, En)
        for (k = 0; k <= 3; k = k+1)
            if ((W == k) && (En == 1))
                Y[k] = 1;
            else
                Y[k] = 0;

endmodule

```


Decoders

Hierarchical code for 4-16 decoder

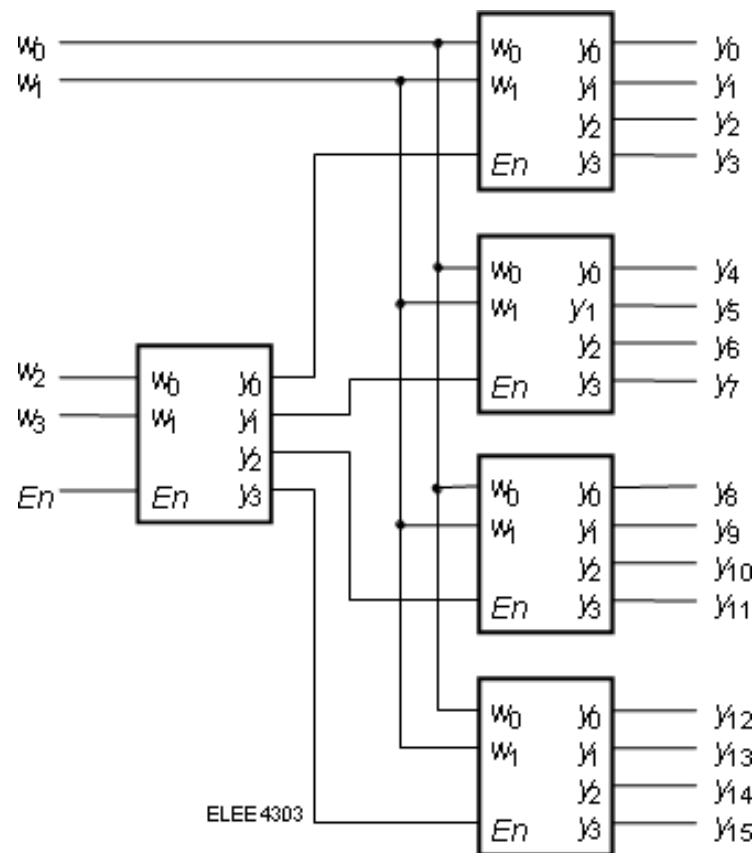


```
module dec4to16 (W, Y, En);
    input [3:0] W;
    input En;
    output [0:15] Y;
    wire [0:3] M;

    dec2to4 Dec1 (W[3:2], M[0:3], En);
    dec2to4 Dec2 (W[1:0], Y[0:3], M[0]);
    dec2to4 Dec3 (W[1:0], Y[4:7], M[1]);
    dec2to4 Dec4 (W[1:0], Y[8:11], M[2]);
    dec2to4 Dec5 (W[1:0], Y[12:15], M[3]);

endmodule
```

Decoders

BCD-to-7-segment decoder

 


```

module seg7 (bcd, leds);
    input [3:0] bcd;
    output [1:7] leds;
    reg [1:7] leds;

    always @(bcd)
        case (bcd) //abcdefg
            0: leds = 7'b1111110;
            1: leds = 7'b0110000;
            2: leds = 7'b1101101;
            3: leds = 7'b1111001;
            4: leds = 7'b0110011;
            5: leds = 7'b1011011;
            6: leds = 7'b1011111;
            7: leds = 7'b1110000;
            8: leds = 7'b1111111;
            9: leds = 7'b1111011;
            default: leds = 7'bx;
        endcase
    endmodule

```

Encoders

 

```
module encoder (Code, Data);  
output[2:0] Code;  
input[7:0] Data;  
reg[2:0] Code;  
  
always@ ( Data )  
    case (Data)  
        8'b00000001 : Code = 3'b000;  
        8'b00000010 : Code = 3'b001;  
        8'b00000100 : Code = 3'b010;  
        8'b00001000 : Code = 3'b011;  
        8'b00010000 : Code = 3'b100;  
        8'b00100000 : Code = 3'b101;  
        8'b01000000 : Code = 3'b110;  
        8'b10000000 : Code = 3'b111;  
        default Code = 3'bx;  
    endcase  
  
endmodule
```

Encoders

Priority encoder using casex

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

```
module priority (W, Y, z);  
    input [3:0] W;  
    output [1:0] Y;  
    output z;  
    reg [1:0] Y;  
    reg z;  
  
    always @(W)  
    begin  
        z = 1;  
        casex(W)  
            4'b1xxx: Y = 3;  
            4'b01xx: Y = 2;  
            4'b001x: Y = 1;  
            4'b0001: Y = 0;  
            default: begin  
                z = 0;  
                Y = 2'bx;  
            end  
        endcase  
    end  
endmodule
```


Encoders

Priority encoder using for loops

w_3	w_2	w_1	w_0	y_1	y_0	z
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	x	0	1	1
0	1	x	x	1	0	1
1	x	x	x	1	1	1

```
module priority (W, Y, z);  
    input [3:0] W;  
    output reg [1:0] Y;  
    output reg z;  
    integer k;  
  
    always @(W)  
    begin  
        Y = 2'bxx;  
        z = 0;  
        for (k = 0; k < 4; k = k+1)  
            if (W[k])  
                begin  
                    Y = k;  
                    z = 1;  
                end  
    end  
  
endmodule
```

Comparators

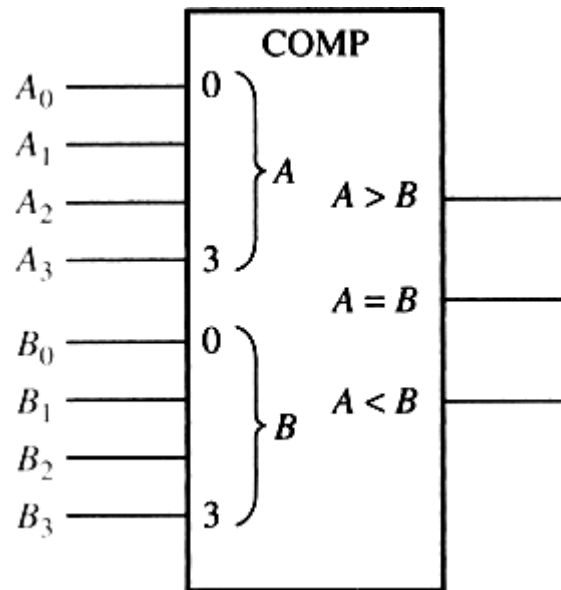

```
module compare (A, B, AeqB, AgtB,AltB);  
  input [3:0] A, B;  
  output reg AeqB, AgtB,AltB;
```

```
  always @(A, B)  
  begin  
    AeqB = 0;  
    AgtB = 0;  
    AltB = 0;  
    if(A == B)  
      AeqB = 1;  
    else if (A > B)  
      AgtB = 1;  
    else  
      AltB = 1;  
  end
```

```
endmodule
```