

# Digital System Design with HDL (I)

## Lecture 8

Dr. Ming Xu and Dr. Kain Lu Low

Dept of Electrical & Electronic Engineering

XJTLU

# In This Session

- Verilog for Sequential Circuits
  - Latches and Flip-Flops
  - Blocking and Non-Blocking Assignments
  - Counters and Registers

# The Latch

## A gated D latch

- Here the always block is sensitive to the **levels** of signals.

```
module D_latch (D, EN, Q);  
    input D, EN;  
    output reg Q;  
  
    always @(D, EN)  
        if (EN)  
            Q = D;  
  
endmodule
```

# Flip-Flops

## A D flip-flop

- Here the always block is sensitive to positive edges (**posedge**) of the signal.

```
module flipflop (D, Clock, Q);  
    input D, Clock;  
    output reg Q;  
  
    always @(posedge Clock)  
        Q = D;  
  
endmodule
```

# Blocking and Non-Blocking Assignments


- **= : Blocking assignments** – evaluate *in order*  
**begin**  
    Q1 = D;  
    Q2 = Q1; // new Q1 goes to Q2.  
**end**
- **<= : No-blocking assignments** – evaluate *in parallel*  
with the variable values when entering **always** block  
**begin**  
    Q1<= D;  
    Q2<= Q1; // old Q1 goes to Q2  
**end**

The order of statements doesn't matter

# Blocking and Non-Blocking Assignments

```
module example7_5 (x1, x2, x3, Clock, f, g);  
  input x1, x2, x3, Clock;  
  output reg f, g;  
  
  always @(posedge Clock)  
  begin  
    f = x1 & x2;  
    g = f | x3;  
  end  
endmodule
```

 
- To reverse the statement order will make significant difference.
- better to combinational circuits.



# Blocking and Non-Blocking Assignments

```
module example7_6 (x1, x2, x3, Clock, f, g);  
  input x1, x2, x3, Clock;  
  output reg f, g;  
  
  always @(posedge Clock)  
  begin  
    f <= x1 & x2;  
    g <= f | x3;  
  end  
  
endmodule
```

 - To reverse the statement order will make no difference.
- better to sequential circuits.



# Flip-Flops

## D flip-flop with asynchronous reset

```
module flipflop (D, Clock, Resetn, Q);  
  input D, Clock, Resetn;  
  output reg Q;  
  
  always @(negedge Resetn or posedge Clock)  
    if (!Resetn)  
      Q <= 0;  
    else  
      Q <= D;  
  
endmodule
```

- **negedge** must be used, because the sensitivity list cannot have both level- and edge-triggered signals.



# Flip-Flops

## D flip-flops with synchronous reset

```
module flipflop (D, Clock, Resetn, Q);  
  input D, Clock, Resetn;  
  output reg Q;  
  
  always @(posedge Clock)  
    if (!Resetn)  
      Q <= 0;  
    else  
      Q <= D;  
  
endmodule
```

# Registers

An n-bit register

```
module regn (D, Clock, Resetn, Q);  
    parameter n = 16;  
    input [n-1:0] D;  
    input Clock, Resetn;  
    output reg [n-1:0] Q;  
  
    always @(negedge Resetn, posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else  
            Q <= D;  
  
endmodule
```

# Shift Registers

A 4-bit shift register

- When load  $L = 1$ , the parallel input  $R$  is loaded.
- When  $L = 0$ , the data are shifted from MSB  $Q_3$  to LSB; Serial input  $w$  is shifted into  $Q_3$ .

```
module shift4 (R, L, w, Clock, Q);  
    input [3:0] R;  
    input L, w, Clock;  
    output reg [3:0] Q;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else  
            begin  
                Q[0] <= Q[1];  
                Q[1] <= Q[2];  
                Q[2] <= Q[3];  
                Q[3] <= w;  
            end  
  
    endmodule
```

# Shift Registers

An n-bit shift register

```
module shiftn (R, L, w, Clock, Q);  
    parameter n = 16;  
    input [n-1:0] R;  
    input L, w, Clock;  
    output reg [n-1:0] Q;  
    integer k;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else  
            begin  
                for (k = 0; k < n-1; k = k+1)  
                    Q[k] <= Q[k+1];  
                Q[n-1] <= w;  
            end  
endmodule
```

# Counters

## A 4-bit up-counter

```
module upcount (Resetn, Clock, E, Q);  
    input Resetn, Clock, E;  
    output reg [3:0] Q;  
  
    always @(negedge Resetn, posedge Clock)  
        if (!Resetn)  
            Q <= 0;  
        else if (E)  
            Q <= Q + 1;  
  
endmodule
```

# Counters

A down-counter with a parallel load

```
module downcount (R, Clock, E, L, Q);  
    parameter n = 8;  
    input [n-1:0] R;  
    input Clock, L, E;  
    output reg [n-1:0] Q;  
  
    always @(posedge Clock)  
        if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q - 1;  
  
endmodule
```

# Counters

An up-down counter

```
module updowncount (R, Clock, L, E, up_down, Q);  
    parameter n = 8;  
    input [n-1:0] R;  
    input Clock, L, E, up_down;  
    output reg [n-1:0] Q;  
    integer direction;  
  
    always @(posedge Clock)  
    begin  
        if (up_down)  
            direction = 1;  
        else  
            direction = -1;  
        if (L)  
            Q <= R;  
        else if (E)  
            Q <= Q + direction;  
    end  
  
endmodule
```