 


# Datapath & Control

---

Readings: 4.1-4.4




Datapath: System for performing operations on data, plus memory access.

Control: Control the datapath in response to instructions.


# Simple CPU

Develop complete CPU for subset of instruction set


Memory: LDUR, STUR

 


Branch: B

 

Conditional Branch: CBZ

 


Arithmetic: ADD, SUB

 

Most other instructions similar

# Execution Cycle

---

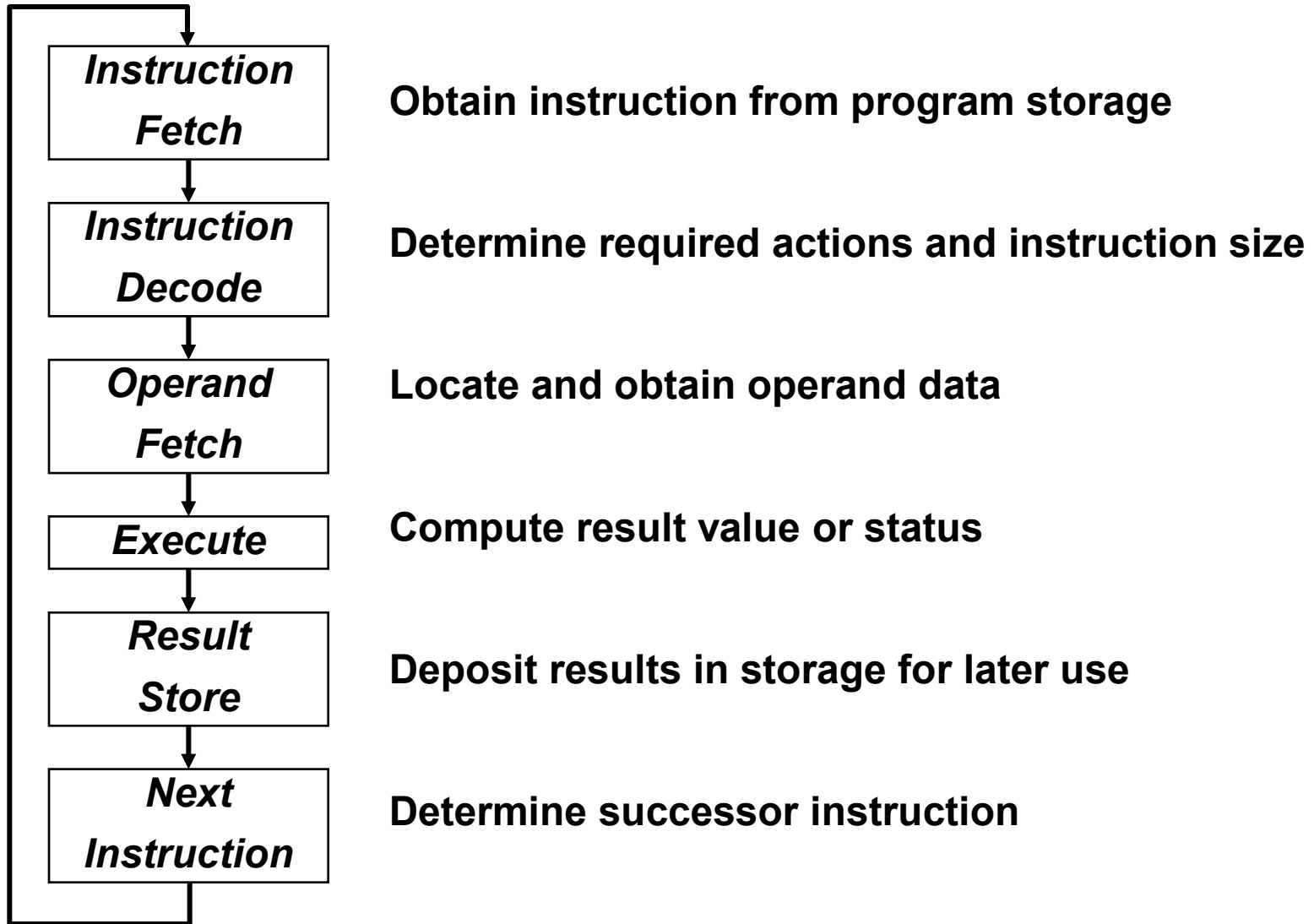

# Processor Overview

---

## Overall Dataflow


PC fetches instructions

Instructions select operand registers, ALU immediate values

ALU computes values

Load/Store addresses computed in ALU

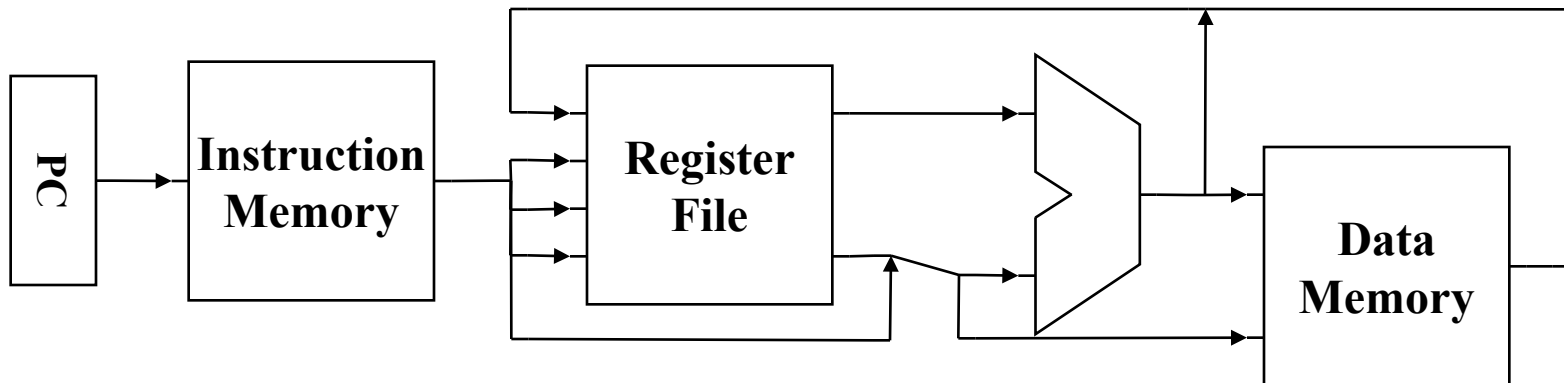Result goes to register file or Data memory



# RTL & Processor Design

---

Convert instructions to Register Transfer Level (RTL) specification

$\text{RegA} = \text{RegB} + \text{RegC};$

RTL specifies required interconnection of units, control



Math unit example:

(add):  $A = A + B; I++;$

(mult):  $A = A * B; I++;$



(hold):  $A = A; I++;$

(init):  $A = \text{Din}; I++;$

  

# Instruction Fetch

---

  


## Add/Subtract RTL

---




Add instruction: ADD Rd, Rn, Rm

Subtract instruction: SUB Rd, Rn, Rm

 

# Add/Subtract Datapath

---

   




# Load RTL


---

Load Instruction: LDUR Rd, [Rn, DAddr9]

 

# Datapath + Load


---

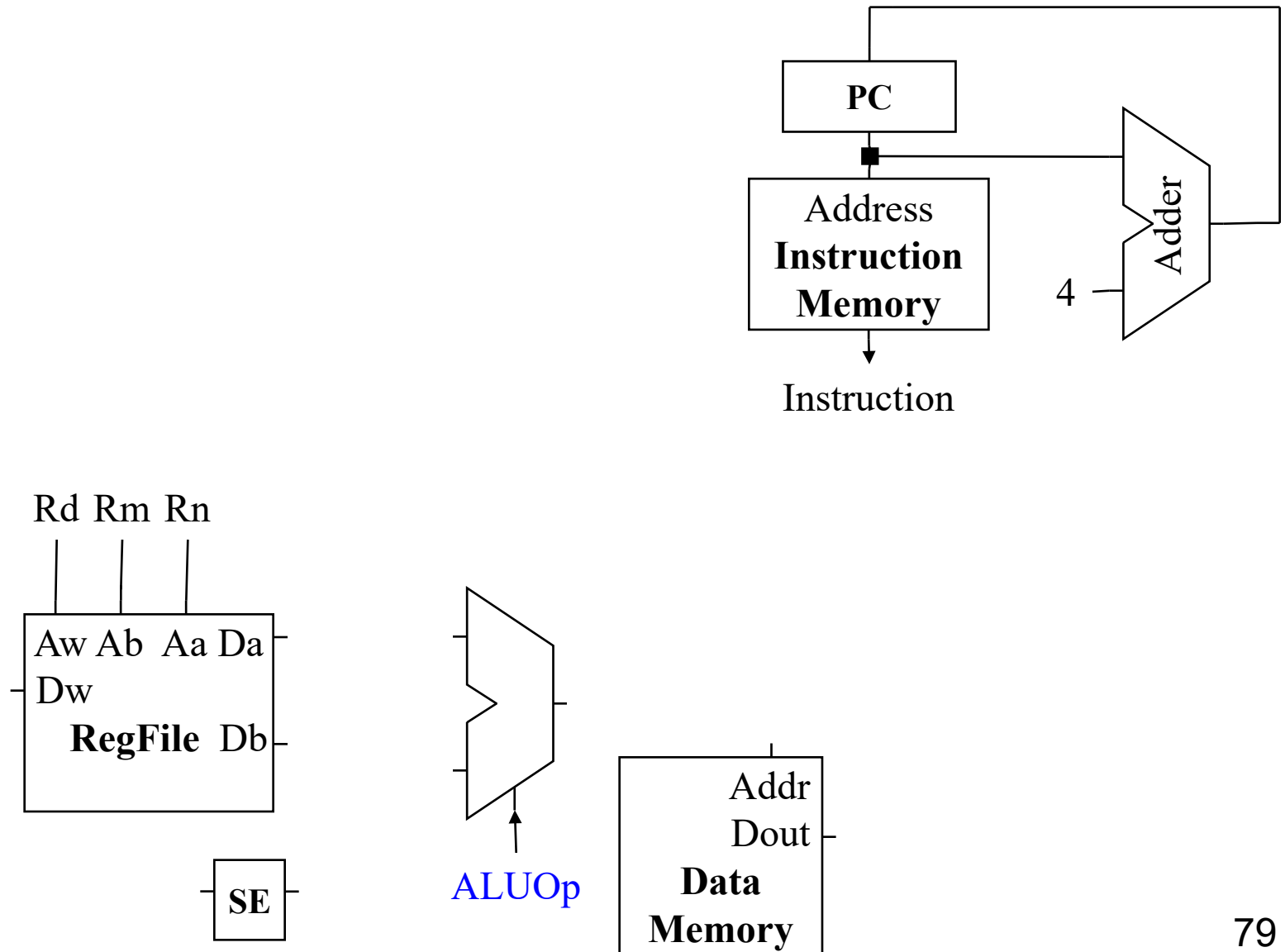


# Store RTL

---

Store Instruction: STUR Rd, [Rn, DAddr9]

 


# Datapath + Store

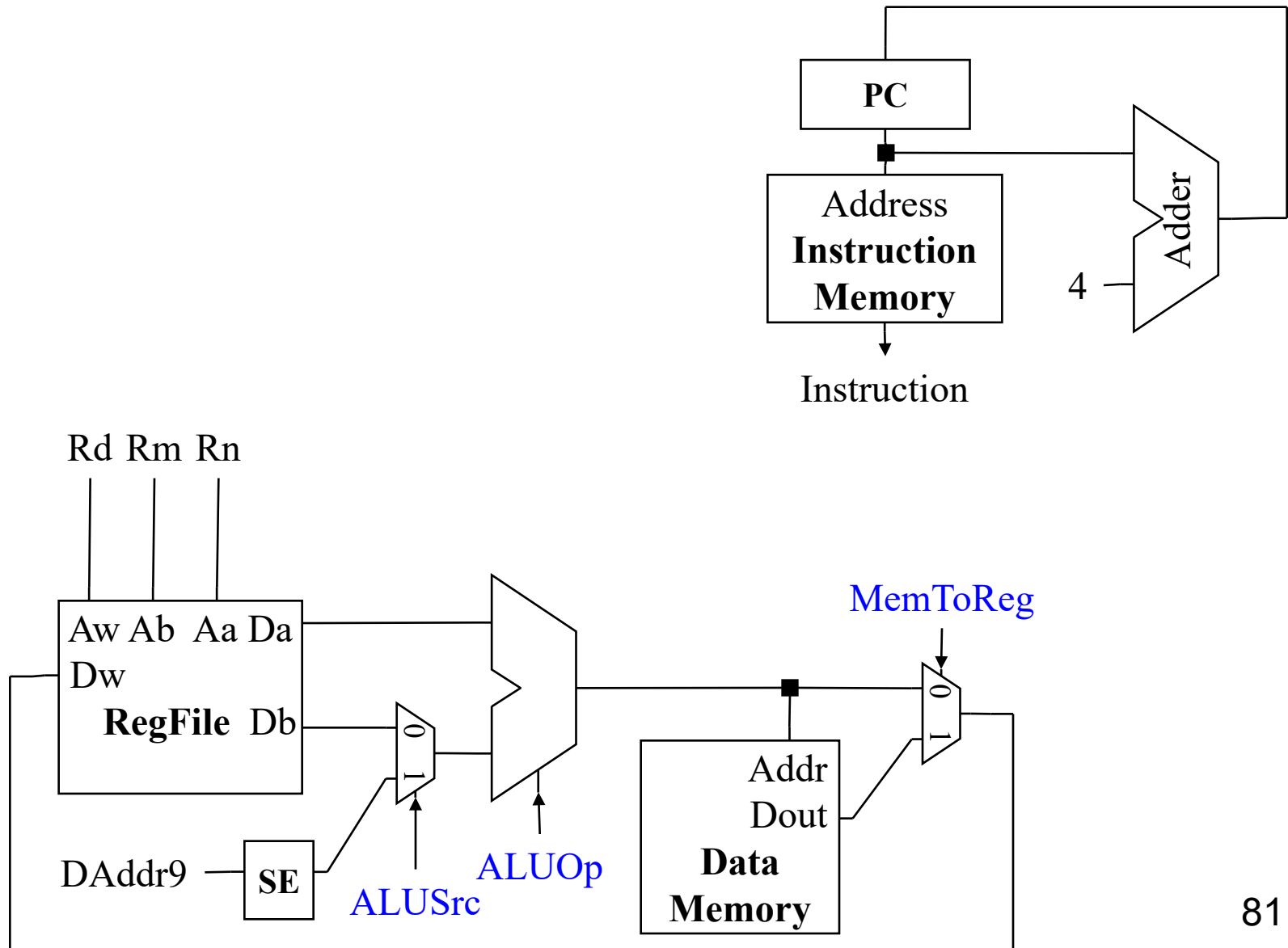


# Branch RTL

---

Branch Instruction: B BrAddr26

 


# Datapath + Branch

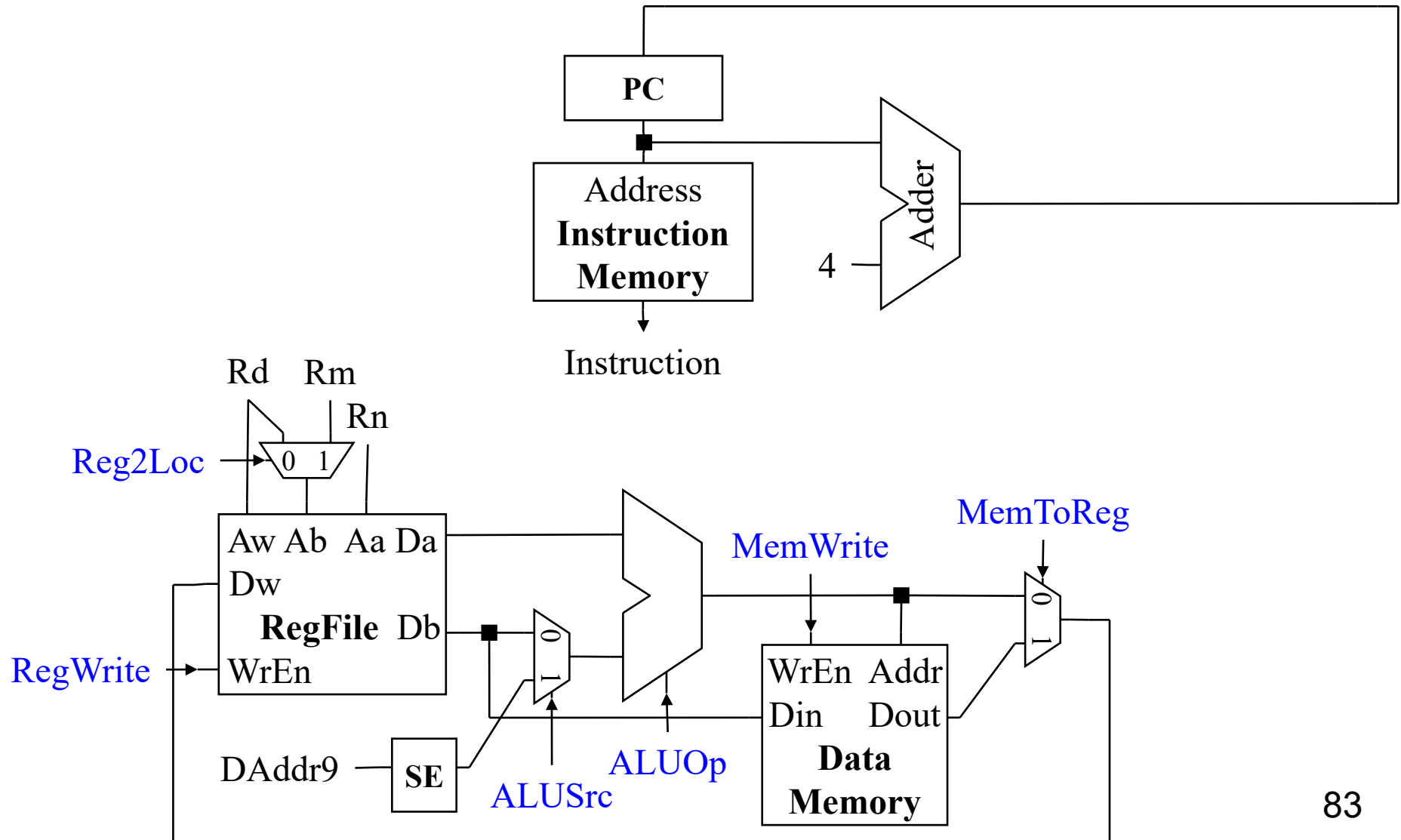

 
# Conditional Branch RTL

---

Conditional Branch Instruction: CBZ Rd, CondAddr19



# Datapath + Conditional Branch

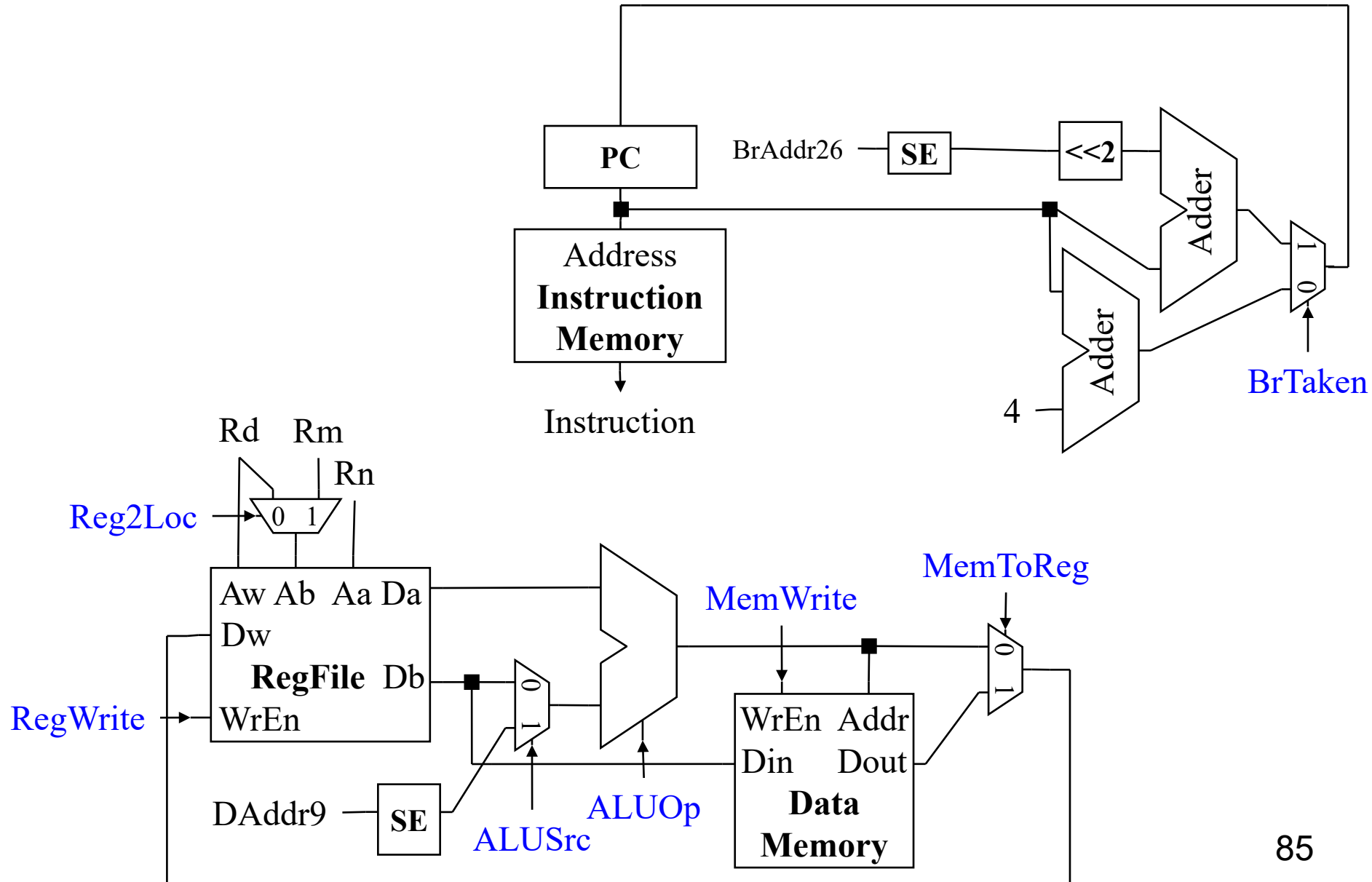



# Control

---

Identify control points for pieces of datapath

- Instruction Fetch Unit

- ALU


- Memories

- Datapath muxes

- Etc.

Use RTL for determine per-instruction control assignments

# Complete Datapath

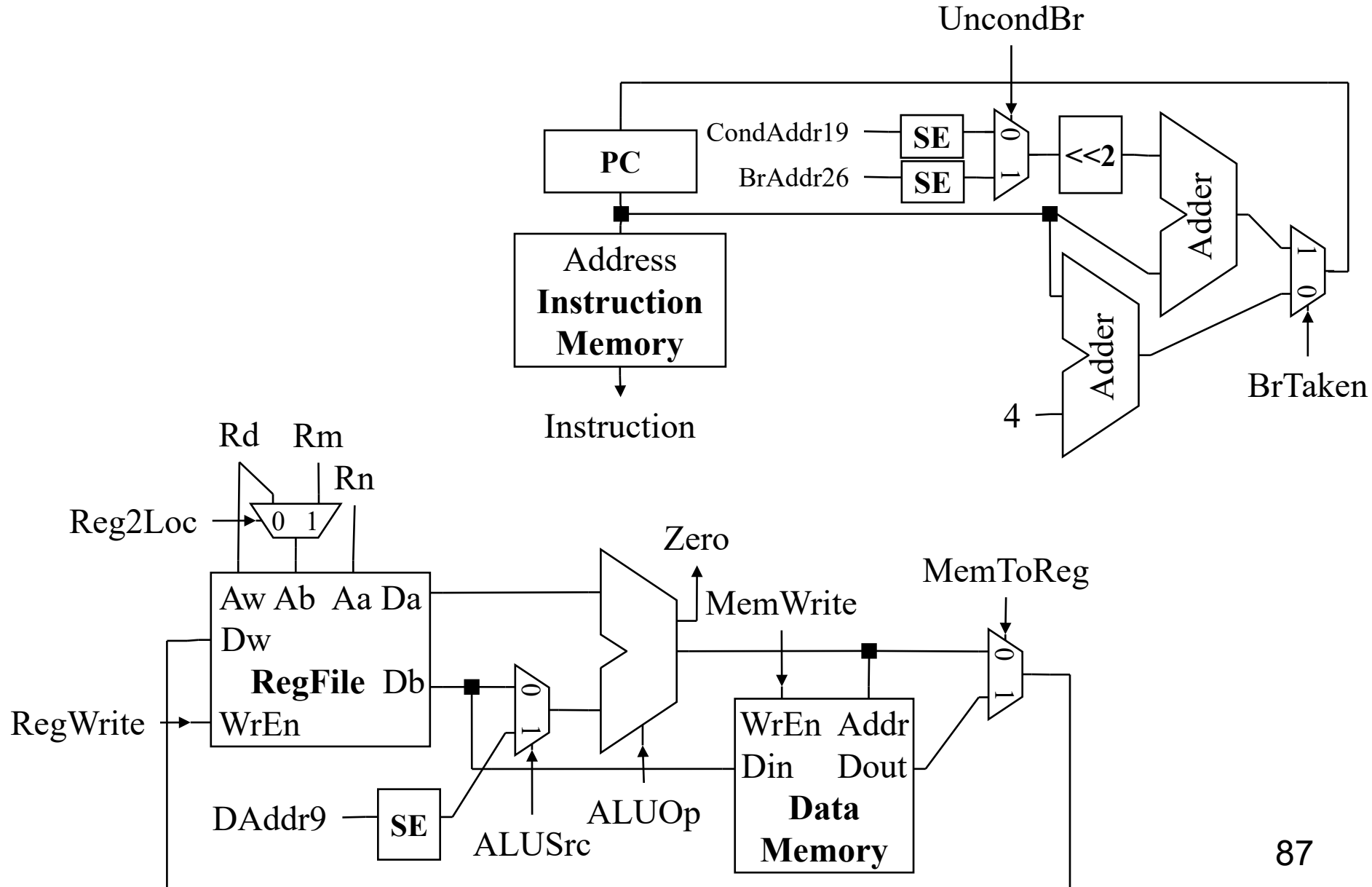


# Control Signals

Opcode[31:26] Opcode[25:21]	100010	110010	111110	111110	000101	101101
	11000	11000	00010	00000	xxxxx	00xxx
	ADD	SUB	LDUR	STUR	B	CBZ
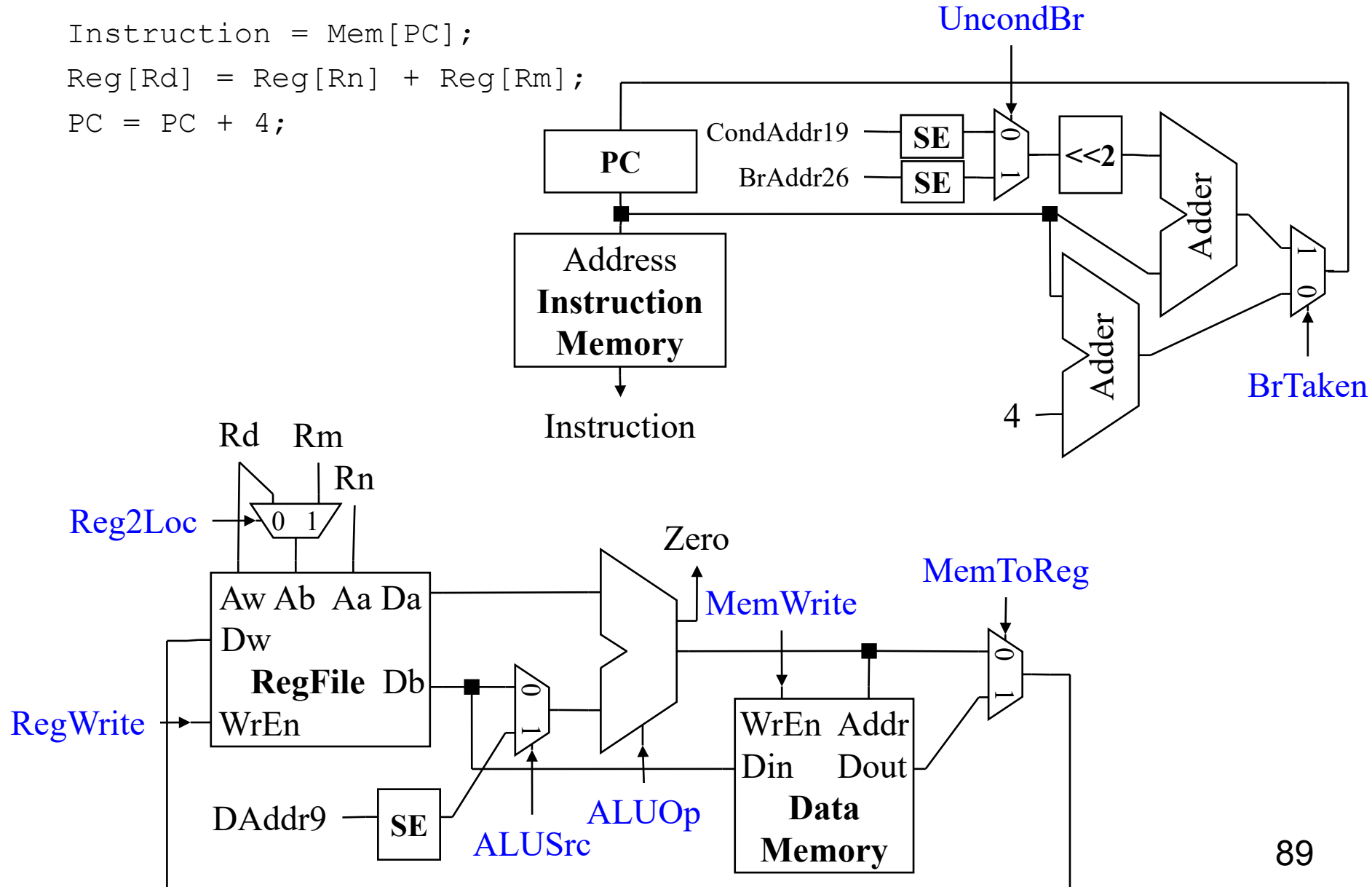
# ADD Control


```
Instruction = Mem[PC];
Reg[Rd] = Reg[Rn] + Reg[Rm];
PC = PC + 4;
```


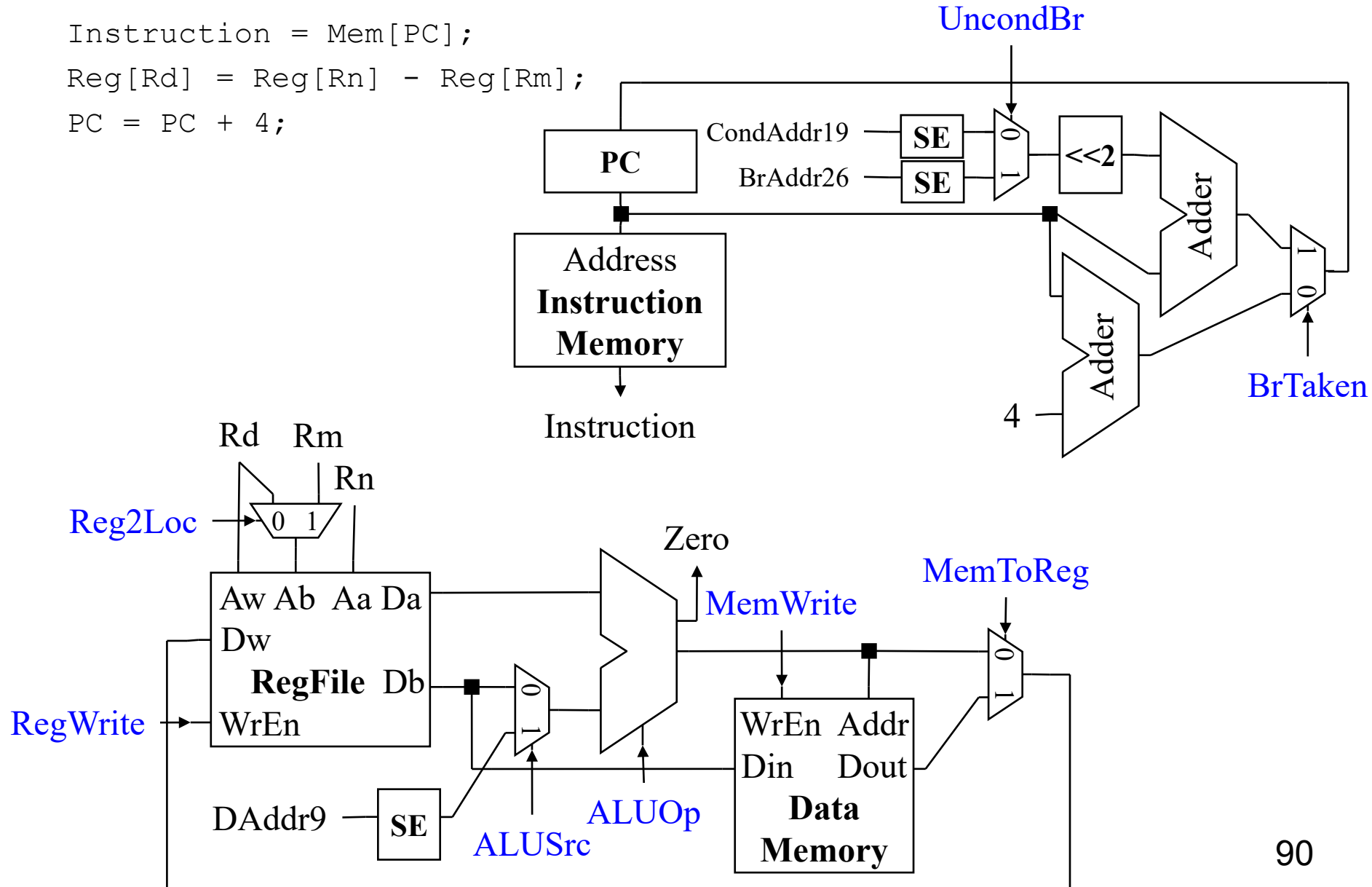
# SUB Control

```

Instruction = Mem[PC];
Reg[Rd] = Reg[Rn] - Reg[Rm];
PC = PC + 4;
    
```




# LDUR Control

Instruction = Mem[PC];

Addr = Reg[Rn] + SignExtend(DAddr9);

Reg[Rd] = Mem[Addr];

PC = PC + 4;

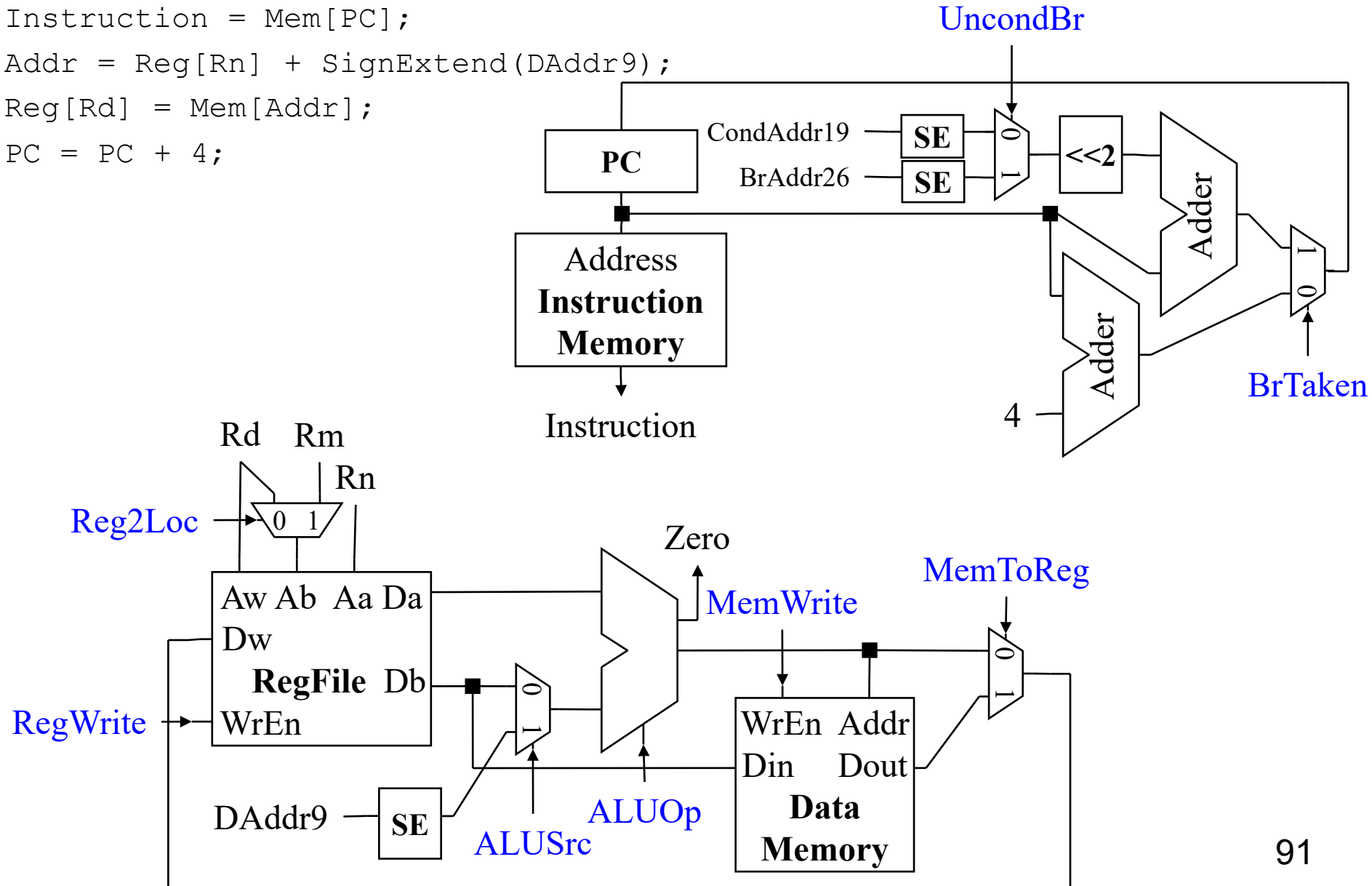


# STUR Control

Instruction = Mem[PC];

Addr = Reg[Rn] + SignExtend(DAddr9);

Mem[Addr] = Reg[Rd];


PC = PC + 4;

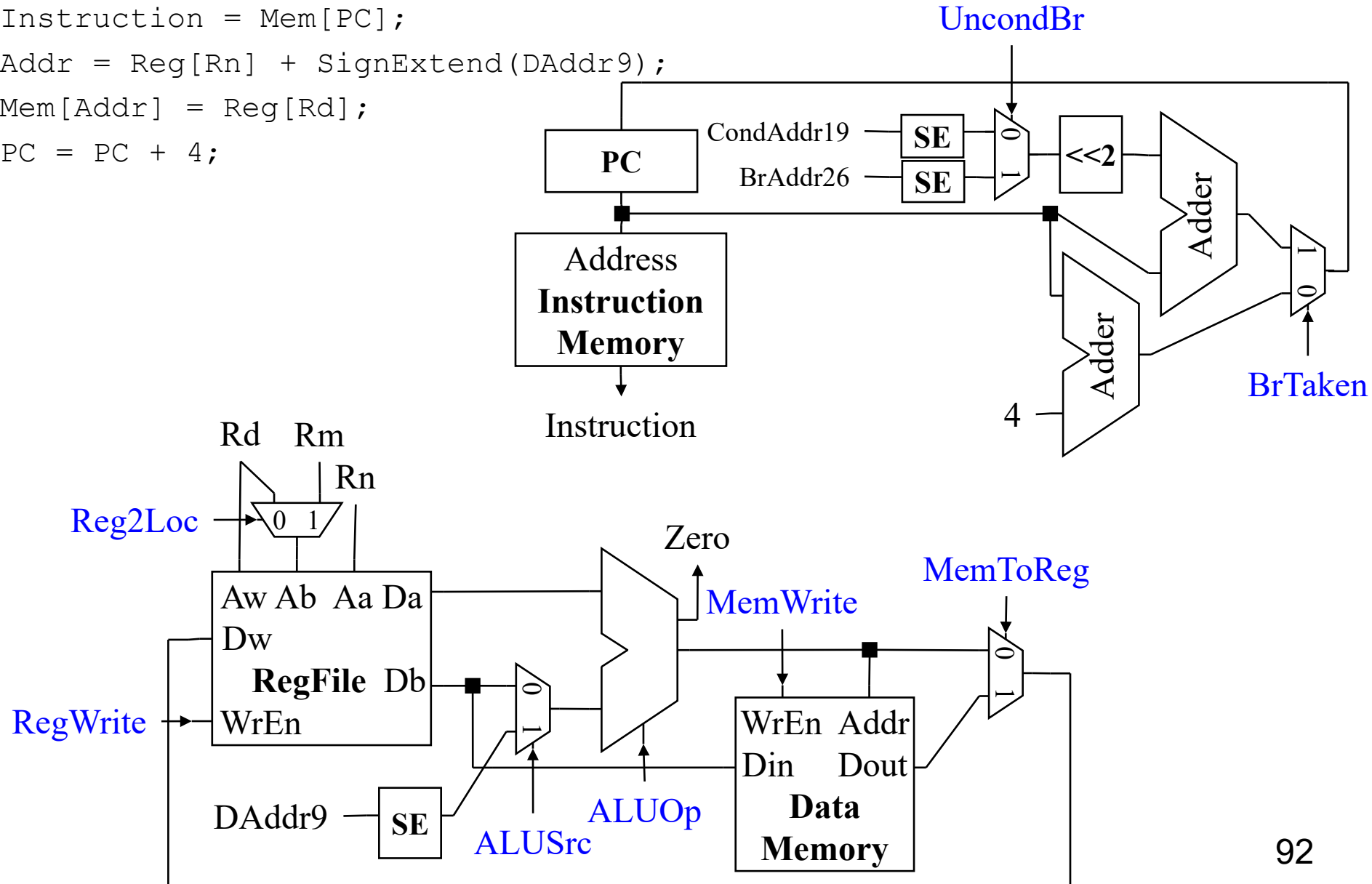

# B Control

Instruction = Mem[PC];

PC = PC + SignExtend(BrAddr26) << 2;

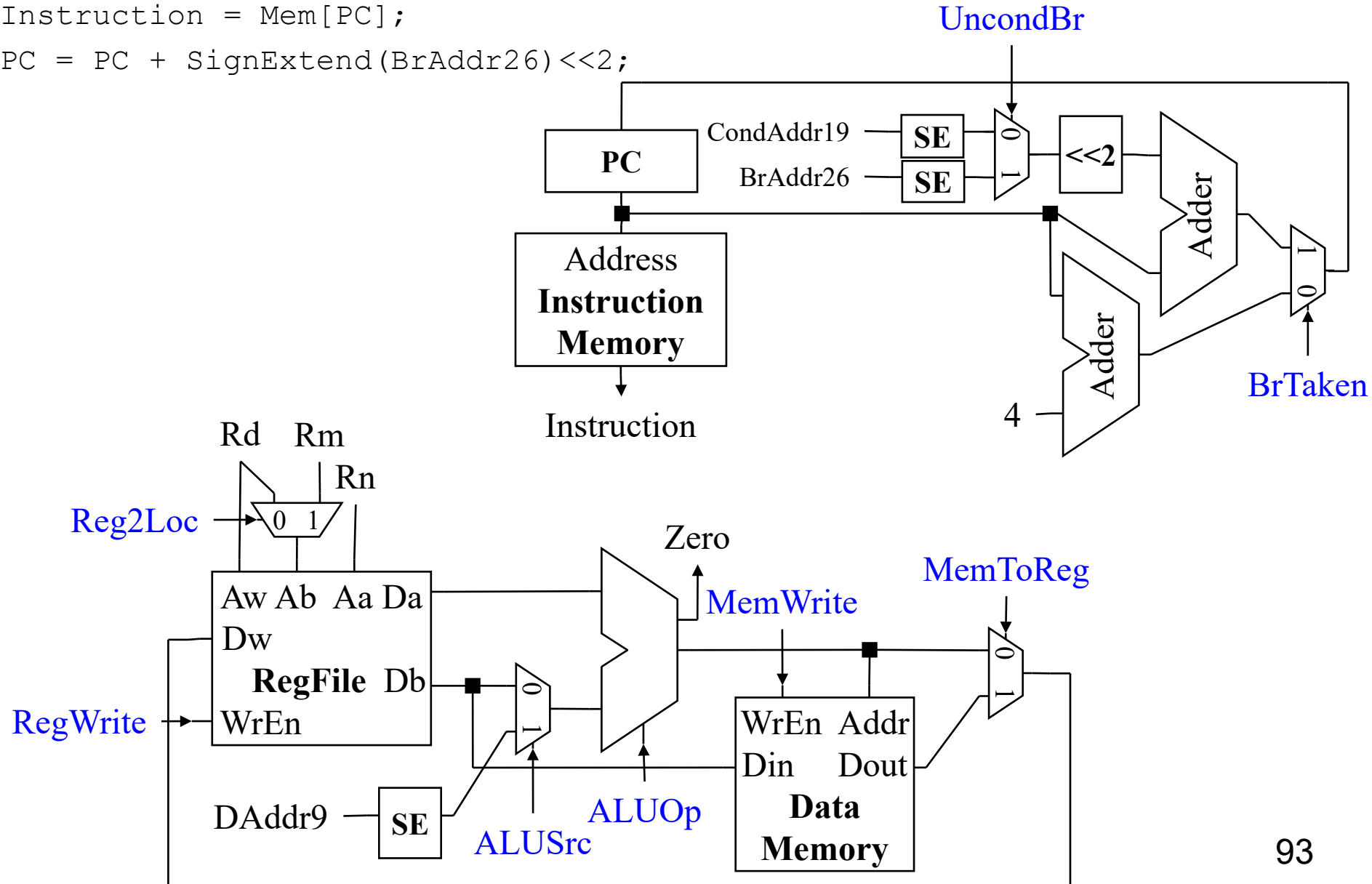



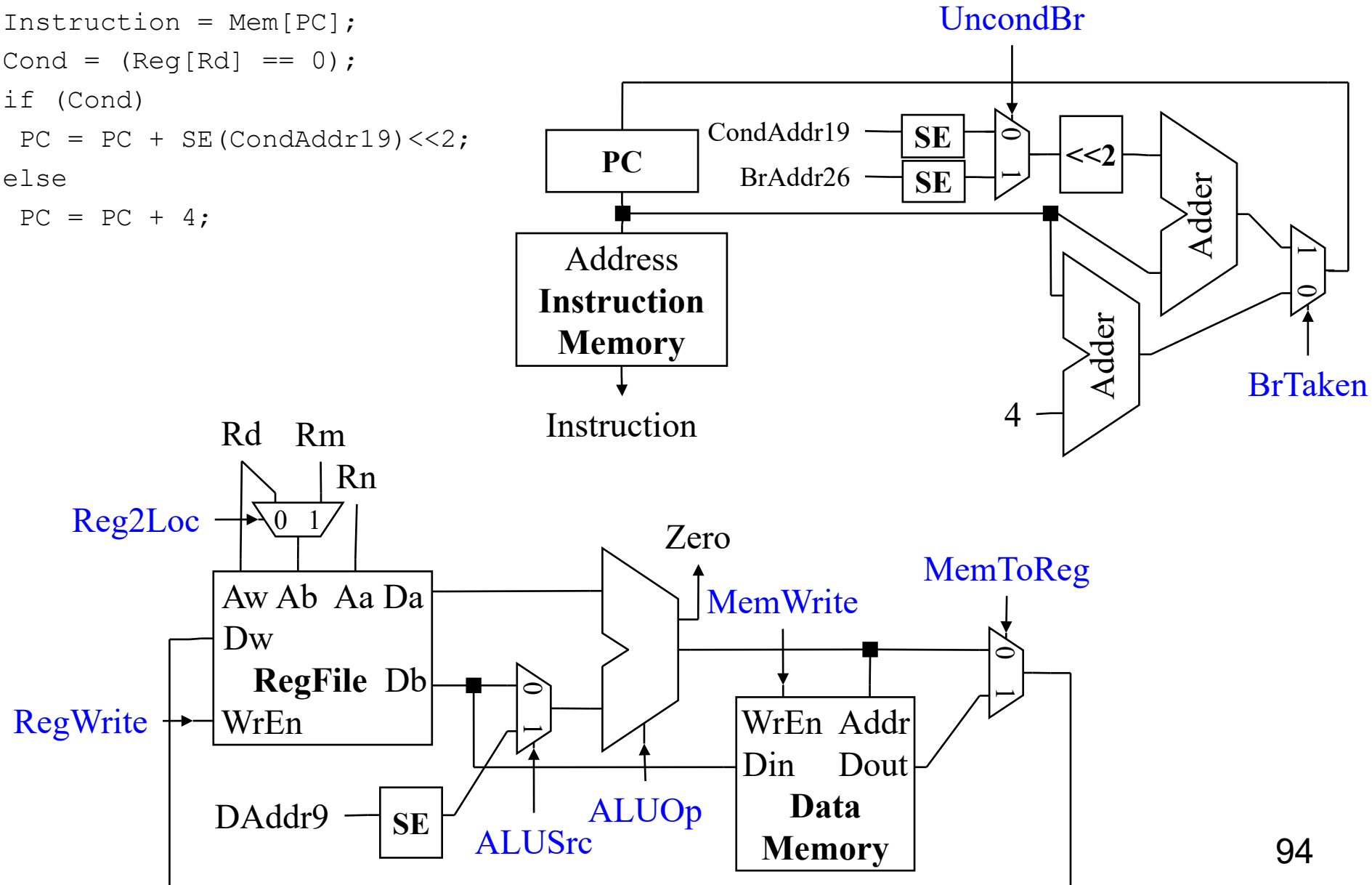
# CBZ Control

```

Instruction = Mem[PC];
Cond = (Reg[Rd] == 0);
if (Cond)
    PC = PC + SE(CondAddr19) << 2;
else
    PC = PC + 4;
    
```



# Advanced: Exceptions


Exception = unusual event in processor

Arithmetic overflow, divide by zero, ...

Call an undefined instruction

Hardware failure

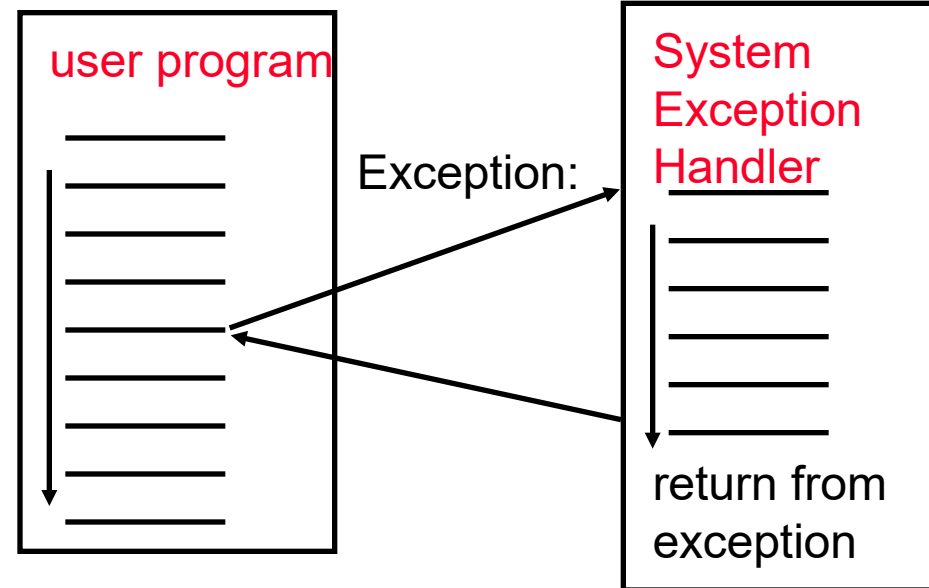I/O device request (called an “interrupt”)



## Approaches

Make software test for exceptional events when they may occur (“polling”)

Have hardware detect these events & react:

Save state (Exception Program Counter, protect the GPRs, note cause)

Call Operating System

If (undef\_instr) PC = C0000000

If (overflow) PC = C0000020

If (I/O) PC = C0000040

...

# Performance of Single-Cycle Machine

---

CPI?

ADD, SUB



LDUR



STUR



CBZ




B


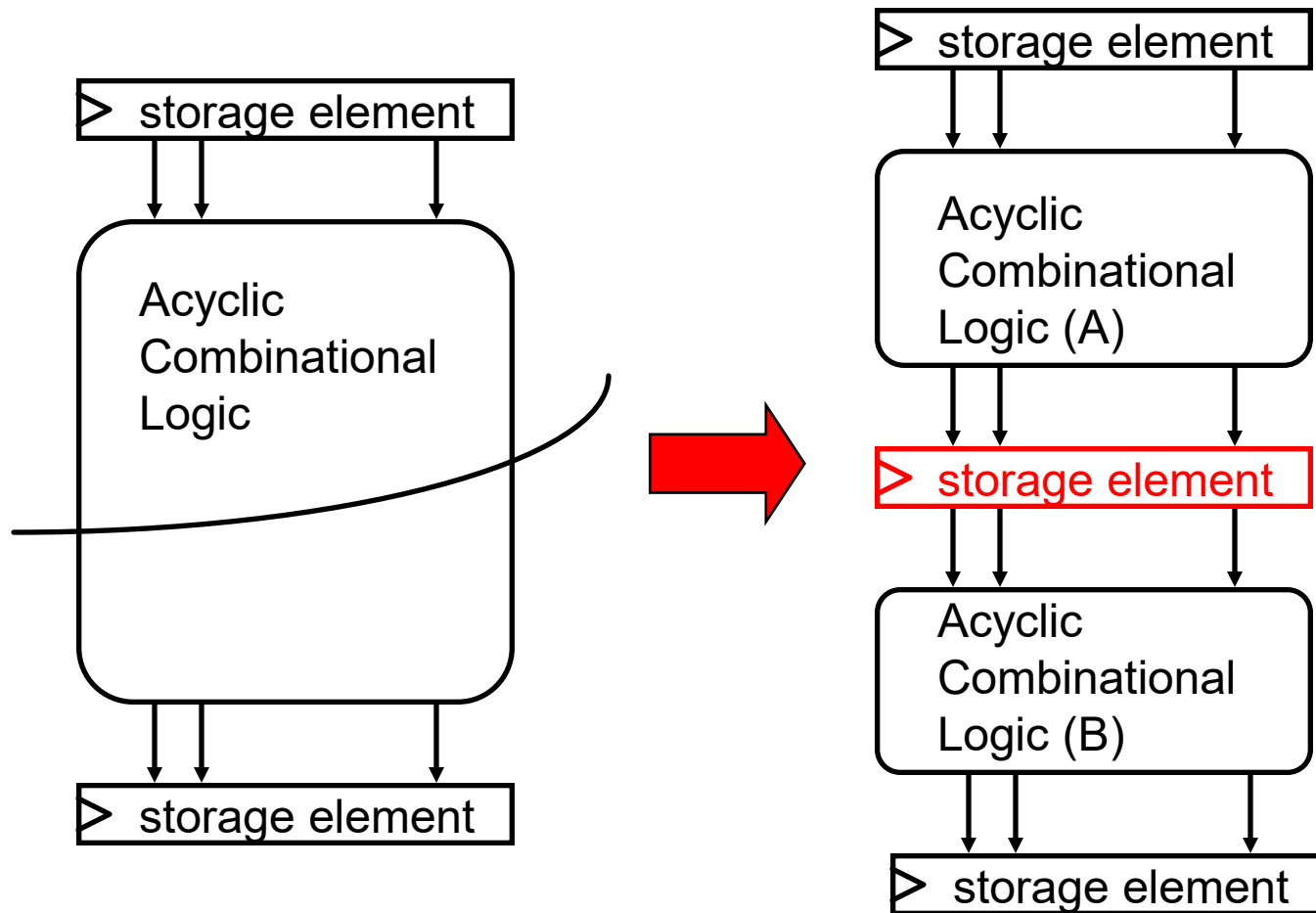
# Reducing Cycle Time

Cut combinational dependency graph and insert register / latch

Do same work in two fast cycles, rather than one slow one



# Pipelined Processor Overview

---

Divide datapath into multiple stages

