Getting Started with HDL

The Nand2Tetris tools that we use in this course represent chips using HDL, a Hardware Description Language. While the HDL language used in this course is a custom variation, Similar languages including VHDL and Verilog are used by chip designers to design, test and validate chips. Such designs can even be programmed into testing chips called FPGAs and be sent for fabrication.

This page is a quickstart guide to Nand2Tetris HDL.

Before you Begin

Make sure you've read the first chapter of the textbook.

{ } HDL Syntax

If you're using a Linux machine in one of the labs, everything is installed and ready-to-go, otherwise you'll need to setup the tools for this course. Follow the steps on the Nand2Tetris Resources (Nand2Tetris Resources (Nand2Tetris Resources/nand2tetris-resources-2 (Nand2Tetris Resources/nand2tetris-resources-2 (<a href="https://myuni.adelaide.edu.au/courses/nan

Note: you must use our version of the nand2tetris tools, found on the page above.

Let's make sure everything works.

- 1. Download the <u>files for Practical Assignment 1</u>
 https://myuni.adelaide.edu.au/courses/101158/files/18016620/wrap=1
 https://myuni.adelaide.edu.au/courses/101158/files/18016620/download?download_frd=1) if you haven't already and unzip them.
- 2. Open a terminal and navigate to the directory containing the files from [1]
- 3. Use the CLI Hardware Simulator and the test script [And.tst] to test the And chip:

```
HardwareSimulator.sh And.tst
```

- This runs the test script on the simulator, produces an output file, And.out and compares it to a file of expected output, And.cmp.
- Does the And chip behave as expected?

- Review the output file, And.out and check how this output compares to what you expect.
- Note: If you're not using the lab PCs, then you'll need to supply the full path to
 HarwareSimulator.sh
- 4. Now try with the GUI Hardware Simulator:

Again, make sure your terminal is in the directory containing the files from [1]

HardwareSimulator.sh

- This should open a user interface that you can use to open and test your HDL files.
- Loading the And.tst script, and running it using the Run >> button.
- Use the view option to see the output and compare values.
- **Note:** Again, if you're not using the lab PCs, then you'll need to supply the full path to HarwareSimulator.sh

Ask your workshop supervisor if you get stuck.

✓ Building your first Chips

We'll start by implementing the Not Chip:

INPUT	OUTPUT	 in	out out
in	out	'''	out
0	1		
1	0		

To do so we'll use a single Nand Chip (our most basic building block in this course):

INF	PUT	OUTPUT	a—out
а	b	out	
0	0	1	
0	1	1	
1	0	1	
1	1	0	

How can we connect the pins of the Nand chip to act in the same way as a Not chip?


1. Edit the Not.hdl file in your preferred editor and attempt to implement the Not chip using a Nand chip. Test your Not chip.

A .hdl file is just a text file and be edited in exactly the same way that you edited your .cpp and .h files in earlier programming courses.

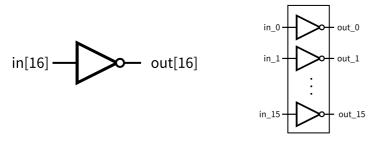- 2. Edit the And hdl file in your preferred editor and attempt to implement the And chip using a Nand chip and your Not chip. Test your And chip.
- 3. Open Gradescope using the link in Practical Assignment 1 and submit your hdl files.

✓ Building your first bus Chips

Bus chips behave like regular chips, except the input and output pins are several bits wide; we represent them as a single pin to simplify our logic:



- 1. Edit the Not16.hdl file in your preferred editor and attempt to implement the 16-bit *Not* chip using multiple *Not* chips. Test your chip.
- 2. Try the same for your And16.hdl file.
- 3. Open Gradescope using the link in Practical Assignment 1 and submit the hdl files.

i Q&A Time

If you have any further questions on "Environments & Jupyter Notebook", clarify them in this workshop.

Prac 1

If you have time left, you can use the remainder of this session to work on your assignments for this week.