

EE304 – Digital Design with HDL (II)

Lecture 15


Verilog for MIPS Processors

Dr. Ming Xu

Dept of Electrical & Electronic Engineering

XJTLU

Single-Cycle Processor

 

```
// MIPS single Cycle processor originaly developed for simulation by Patterson and  
Hennesy  
// Modified for synthesis using the Quartus II package by Dr. S. Ami-Nejad. Feb. 2009
```

// Register File

```
module RegisterFile (Read1,Read2,Writereg,WriteData,RegWrite, Data1,  
Data2,clock,reset);
```

```
    input  [4:0] Read1,Read2,Writereg; // the registers numbers to read or write  
    input  [31:0] WriteData;    // data to write  
    input  RegWrite; // The write control  
    input  clock, reset; // The clock to trigger writes  
    output [31:0] Data1, Data2; // the register values read;  
    reg    [31:0] RF[31:0]; // 32 registers each 32 bits long  
    integer k;
```

```
    // Read from registers independent of clock
```

```
    assign Data1 = RF[Read1];
```

```
    assign Data2 = RF[Read2];
```

```
    always @(posedge clock or posedge reset)
```

```
        if (reset) for(k=0;k<32;k=k+1) RF[k]<=32'h00000000;
```

```
        // Register 0 is a read only register with the content of 0
```

```
        else      if (RegWrite & (Writereg!=0)) RF[Writereg] <= WriteData;
```

```
endmodule
```

//ALU Control

```
module ALUControl (ALUOp, FuncCode, ALUCtl);
```

```
    input [1:0]    ALUOp;  
    input [5:0]    FuncCode;  
    output[3:0]    ALUCtl;  
    reg            [3:0]    ALUCtl;
```

```
    always@( ALUOp, FuncCode)
```

```
    begin
```

```
        case(ALUOp)
```

```
            2'b00:ALUCtl = 4'b0010;
```

```
            2'b01:ALUCtl = 4'b0110;
```

```
            2'b10:case(FuncCode)
```

```
                6'b 100000: ALUCtl = 4'b 0010;
```

```
                6'b 100010: ALUCtl = 4'b 0110;
```

```
                6'b 100100: ALUCtl = 4'b 0000;
```

```
                6'b 100101: ALUCtl = 4'b 0001;
```

```
                6'b 101010: ALUCtl = 4'b 0111;
```

```
                default:  ALUCtl = 4'b xxxx;
```

```
            endcase
```

```
        default:  ALUCtl = 4'b xxxx;
```

```
        endcase
```

```
    end
```

```
endmodule
```

//ALU

```
module MIPSALU (ALUctl, A, B, ALUOut, Zero);
```

```
    input [3:0]    ALUctl;
```

```
    input [31:0]   A,B;
```

```
    output[31:0]   ALUOut;
```

```
    output         Zero;
```

```
    reg            [31:0] ALUOut;
```

```
    assign Zero = (ALUOut==0); //Zero is true if ALUOut is 0
```

```
    always @(ALUctl, A, B) begin //reevaluate if these change
```

```
    case (ALUctl)
```

```
        0: ALUOut <= A & B;
```

```
        1: ALUOut <= A | B;
```

```
        2: ALUOut <= A + B;
```

```
        6: ALUOut <= A - B;
```

```
        7: ALUOut <= A < B ? 1:0;
```

```
        // .... Add more ALU operations here
```

```
        default: ALUOut <= A;
```

```
    endcase
```

```
    end
```

```
endmodule
```

// Data Memory

```
module DataMemory(Address, DWriteData, MemRead, MemWrite, clock, reset,  
DReadData);
```

```
input    [31:0]    Address, DWriteData;  
input    MemRead, MemWrite, clock, reset;  
output   [31:0]    DReadData;  
reg      [31:0]    DMem[7:0];
```

```
assign DReadData = DMem[Address[2:0]];  
always @(posedge clock or posedge reset)begin  
    if (reset) begin
```

```
        DMem[0]=32'h00000005;  
        DMem[1]=32'h0000000A;  
        DMem[2]=32'h00000055;  
        DMem[3]=32'h000000AA;  
        DMem[4]=32'h00005555;  
        DMem[5]=32'h00008888;  
        DMem[6]=32'h00550000;  
        DMem[7]=32'h00004444;  
    end else  
        if (MemWrite) DMem[Address[2:0]] <= DWriteData;
```

```
    end  
endmodule
```

// Main Controller

```
module Control
(opcode,RegDst,Branch,MemRead,MemtoReg,ALUOp,MemWrite,ALUSrc,RegWrite);
input    [5:0]    opcode;
output   [1:0]    ALUOp;
output   RegDst,Branch,MemRead,MemtoReg,MemWrite,ALUSrc,RegWrite;
reg      [1:0]    ALUOp;
reg      RegDst,Branch,MemRead,MemtoReg,MemWrite,ALUSrc,RegWrite;

parameter R_Format = 6'b000000, LW = 6'b100011, SW = 6'b101011,
BEQ=6'b000100;
always @(opcode)begin
    case(opcode)
        R_Format:{RegDst,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,
Branch,ALUOp}= 9'b 100100010;
        LW:      {RegDst,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,
Branch,ALUOp}= 9'b 011110000;
        SW:      {RegDst,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,
Branch,ALUOp}= 9'b x1x001000;
        BEQ:     {RegDst,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,
Branch,ALUOp}= 9'b x0x000101;
        default: {RegDst,ALUSrc,MemtoReg,RegWrite,MemRead,MemWrite,
Branch,ALUOp}= 9'b xxxxxxxxx;
    endcase
end
endmodule
```

// Datapath (Part 1)

```
module DataPath(RegDst, Branch, MemRead, MemtoReg, ALUOp, MemWrite,  
ALUSrc, RegWrite, clock, reset, opcode,/* RF1, RF2,  
RF3,*/ALUResultOut ,DReadData);
```

```
input      RegDst,Branch,MemRead,MemtoReg,MemWrite,ALUSrc,RegWrite,clock,  
reset;
```

```
input      [1:0]      ALUOp;
```

```
output     [5:0]      opcode;
```

```
output     [31:0]     /*RF1, RF2, RF3,*/ ALUResultOut ,DReadData;
```

```
reg        [31:0] PC, IMemory[0:31];
```

```
wire       [31:0] SignExtendOffset, PCOffset, PCValue, ALUResultOut,  
            IAddress, DAddress, IMemOut, DmemOut, DWriteData, Instruction,  
            RWriteData, DReadData, ALUAin, ALUBin;
```

```
wire       [3:0] ALUctl;
```

```
wire       Zero;
```

```
wire       [4:0] WriteReg;
```

```
//Instruction fields, to improve code readability
```

```
wire [5:0] funct;
```

```
wire [4:0] rs, rt, rd, shamt;
```

```
wire [15:0] offset;
```


// Datapath (Part 2)

//Instantiate local ALU controller

ALUControl alucontroller(ALUOp,funct,ALUctl);

// Instantiate ALU

MIPSA LU ALU(ALUctl, ALUAin, ALUBin, ALUResultOut, Zero);

// Instantiate Register File

RegisterFile REG(rs, rt, WriteReg, RWriteData, RegWrite, ALUAin, DWriteData,clock,reset);

// Instantiate Data Memory

DataMemory datamemory(ALUResultOut, DWriteData, MemRead, MemWrite, clock, reset, DReadData);

// Instantiate Instruction Memory

IMemory IMemory_inst (
 .address (PC[6:2]),
 .q (Instruction)
);

// Datapath (Part 3)

// Synthesize multiplexers

```
assign WriteReg = (RegDst) ? rd : rt;
```

```
assign ALUBin = (ALUSrc) ? SignExtendOffset : DWriteData;
```

```
assign PCValue = (Branch & Zero) ? PC+4+PCOffset : PC+4;
```

```
assign RWriteData = (MemtoReg) ? DReadData : ALUResultOut;
```

// Acquire the fields of the R_Format Instruction for clarity

```
assign {opcode, rs, rt, rd, shamt, funct} = Instruction;
```

// Acquire the immediate field of the I_Format instructions

```
assign offset = Instruction[15:0];
```

//sign-extend lower 16 bits

```
assign SignExtendOffset = { {16{offset[15]}} , offset[15:0]};
```

// Multiply by 4 the PC offset

```
assign PCOffset = SignExtendOffset << 2;
```

// Write the address of the next instruction into the program counter

```
always @(posedge clock ) begin
```

```
if (reset) PC<=32'h00000000; else
```

```
    PC <= PCValue;
```

```
end
```

```
endmodule
```

// Processor


```
module MIPS1CYCLE(clock, reset, opcode, ALUResultOut ,DReadData);
    input clock,      reset;
    output[5:0]       opcode;
    output[31:0]      ALUResultOut ,DReadData; // For simulation purposes

    wire [1:0] ALUOp;
    wire [5:0] opcode;
    wire [31:0] SignExtend,ALUResultOut ,DReadData;
    wire RegDst,Branch,MemRead,MemtoReg,MemWrite,ALUSrc,RegWrite;

    // Instantiate the Datapath
    DataPath MIPS1CYCLE (RegDst,Branch,MemRead,MemtoReg,ALUOp,
        MemWrite,ALUSrc,RegWrite,clock, reset, opcode, ALUResultOut ,DReadData);

    //Instantiate the combinational control unit
    Control MIPSControl (opcode,RegDst,Branch,MemRead,MemtoReg,ALUOp,
        MemWrite,ALUSrc,RegWrite);
endmodule
```

Multi-Cycle Processor

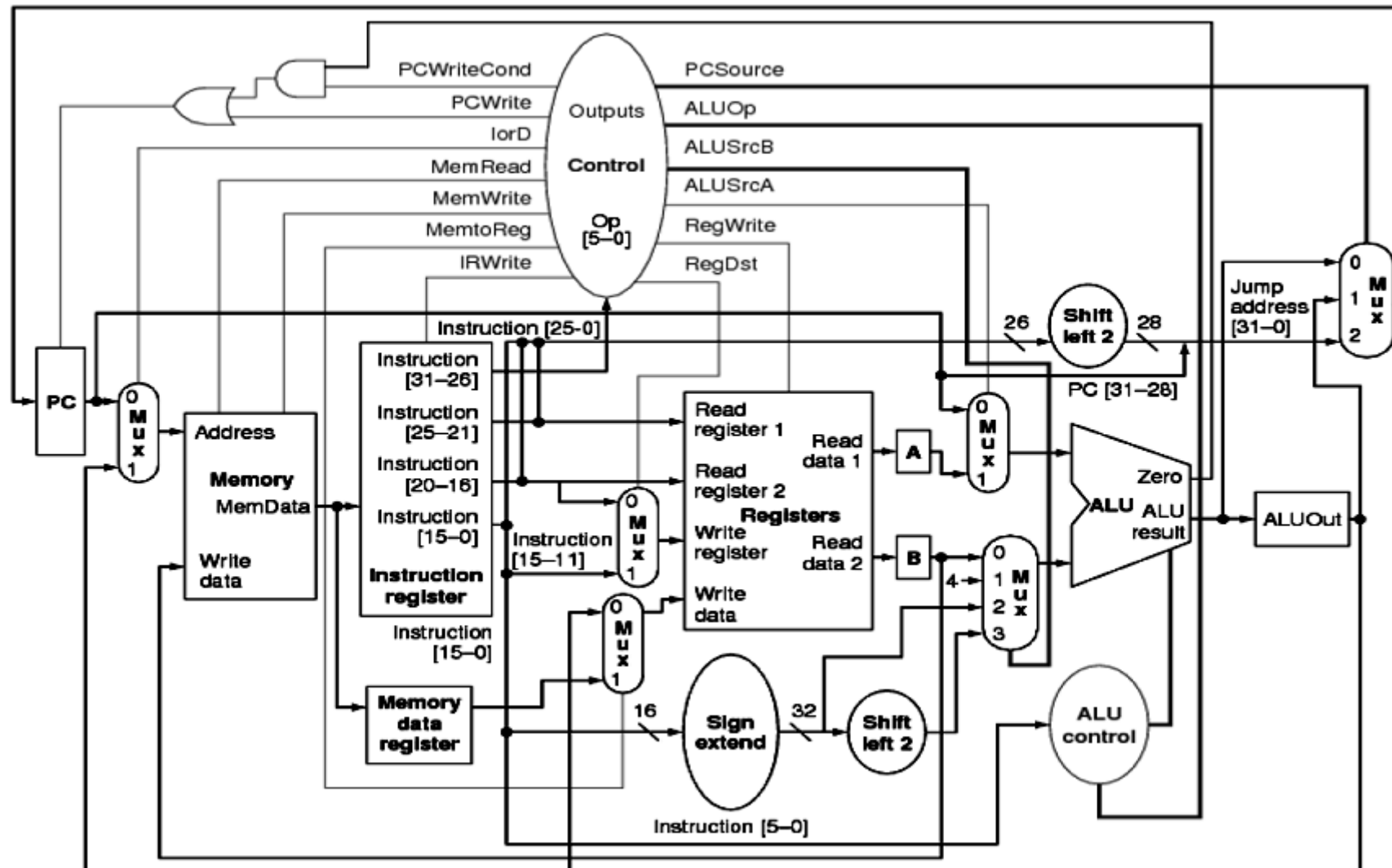

// Part 1

// The behavioural specification of a MIPS multicycle processor originally developed for simulation by Patterson and Hennesy

// Modified by Dr. M. Xu in June 2010

```
module CPU (clock, reset);
```

```
parameter R_Type = 6'b000000, LW = 6'b100011, SW = 6'b101011, BEQ=6'b000100,  
J=6'000010;
```

```
input clock, reset; //external inputs
```

```
// The architecturally visible registers and scratch registers for implementation
```

```
reg [31:0] PC, Regs[0:31], Memory [0:31], IR, ALUOut, MDR, A, B;
```

```
reg [2:0] state; // processor state
```

```
wire [5:0] opcode; //use to get opcode easily
```

```
wire [31:0] SignExtend,PCOffset; //used to get sign extended offset field
```

```
assign opcode = IR[31:26]; //opcode is upper 6 bits
```

```
assign SignExtend = {{16{IR[15]}},IR[15:0]}; //sign extension of lower 16-bits of  
instruction
```

```
assign PCOffset = SignExtend << 2; //PC offset is shifted
```

```
// set the PC to 0 and start the control in state 1
```

```
initial begin PC = 0; state = 1; end
```

// Part 2

```
//The state machine--triggered on a rising clock  
always @(posedge clock or posedge reset) begin  
  Regs[0] = 0; // to make sure R0 is always 0
```

```
  if (reset) begin
```

```
    PC = 0;
```

```
    state = 1;
```

```
    Memory[16]=32'h00000005; // words 16-31 used for data memory
```

```
    Memory[17]=32'h0000000B; // words 0-15 used for instruction memory
```

```
    Memory[18]=32'h00000055;
```

```
    Memory[19]=32'h000000BB;
```

```
    Memory[20]=32'h00005555;
```

```
    Memory[21]=32'h0000BBBB;
```

```
    Memory[22]=32'h55555555;
```

```
    Memory[23]=32'hBBBBBBBB;
```

```
    // add the machine code of your instructions here
```

```
  end
```

```
  case (state) //action depends on the state
```

```
    1: begin // first step: fetch the instruction, increment PC, go to next state
```

```
      IR <= Memory[PC>>2];
```

```
      PC <= PC + 4;
```

```
      state=2; //next state
```

```
    end
```

// Part 3

2: begin // second step: Instruction decode, register fetch, also branch address

A <= Regs[IR[25:21]];

B <= Regs[IR[20:16]];

state= 3;

ALUOut <= PC + PCOffset; // compute PC-relative branch target

end

3: begin // third step: Load/store execution, ALU execution, Branch completion

state =4; // default next state

if ((opcode==LW) |(opcode==SW)) ALUOut <= A + SignExtend; // memory address

else if (opcode == R_Type) case (IR[5:0]) //case for the various R-type instructions

32: ALUOut= A + B; //add operation

default: ALUOut= A; //other R-type operations: subtract, SLT, etc.

endcase

else if (opcode == BEQ) begin

if (A==B) PC <= ALUOut; // branch taken--update PC

state = 1;

end

else if (opcode == J) begin

PC = {PC[31:28], IR[25:0],2'b00}; // the jump target PC

state = 1;

end //Jumps

else ; // other opcodes or exception for undefined instruction would go here

end

// Part 4

4: begin

if (opcode == R_Type) begin //ALU Operation

Regs[IR[15:11]] <= ALUOut; // write the result

state = 1;

end //R-type finishes

else if (opcode == LW) begin // load instruction

MDR <= Memory[ALUOut>>2]; // read the memory

state = 5; // next state

end

else if (opcode == SW) begin

Memory[ALUOut>>2] <= B; // write the memory

state = 1; // return to state 1

end //store finishes

else ; // other instructions go here

end

5: begin // LW is the only instruction still in execution

Regs[IR[20:16]] = MDR; // write the MDR to the register

state = 1;

end //complete a LW instruction

endcase

end

endmodule