

Digital System Design with HDL (I)

Lecture 11

Dr. Ming Xu and Dr. Kain Lu Low


Dept of Electrical & Electronic Engineering

XJTLU

In This Session


- Moore-Type FSMs
- Mealy-Type FSMs
- Verilog Code for FSMs

General Form of A Sequential Circuit.

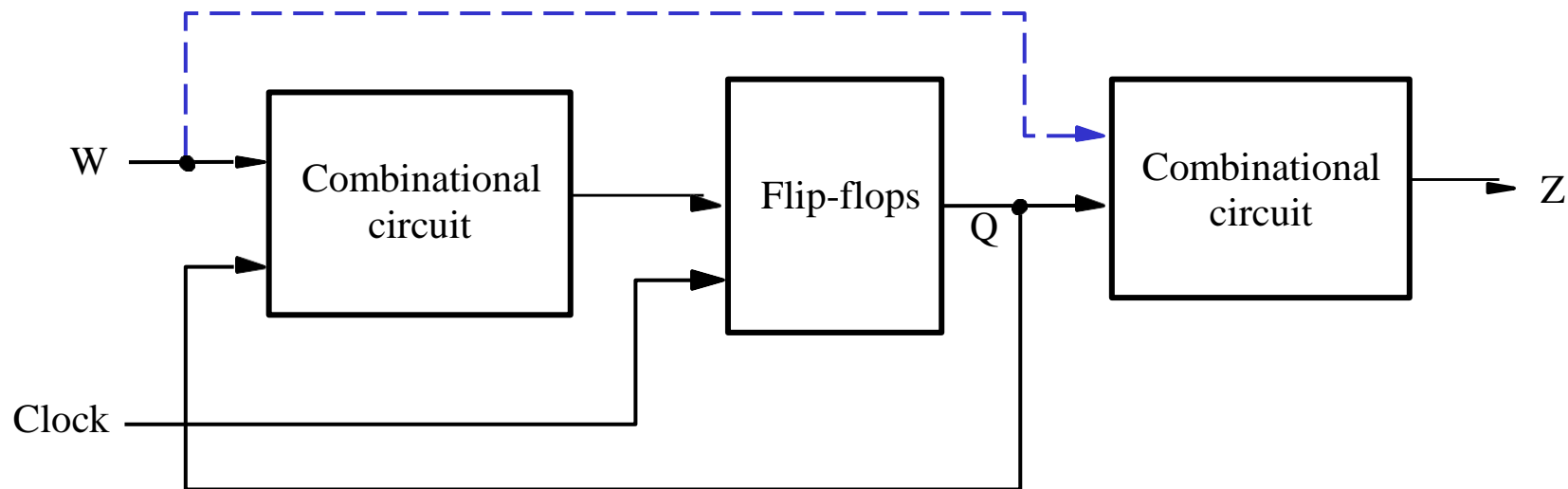

- Sequential circuits are called **finite state machines (FSM)**.
- Combinational circuit 1 has inputs from the input W and the state Q of the flip-flops.
- The output Z always depends on the state Q of the flip-flops. It may also depend on the input W .

General Form of A Sequential Circuit.

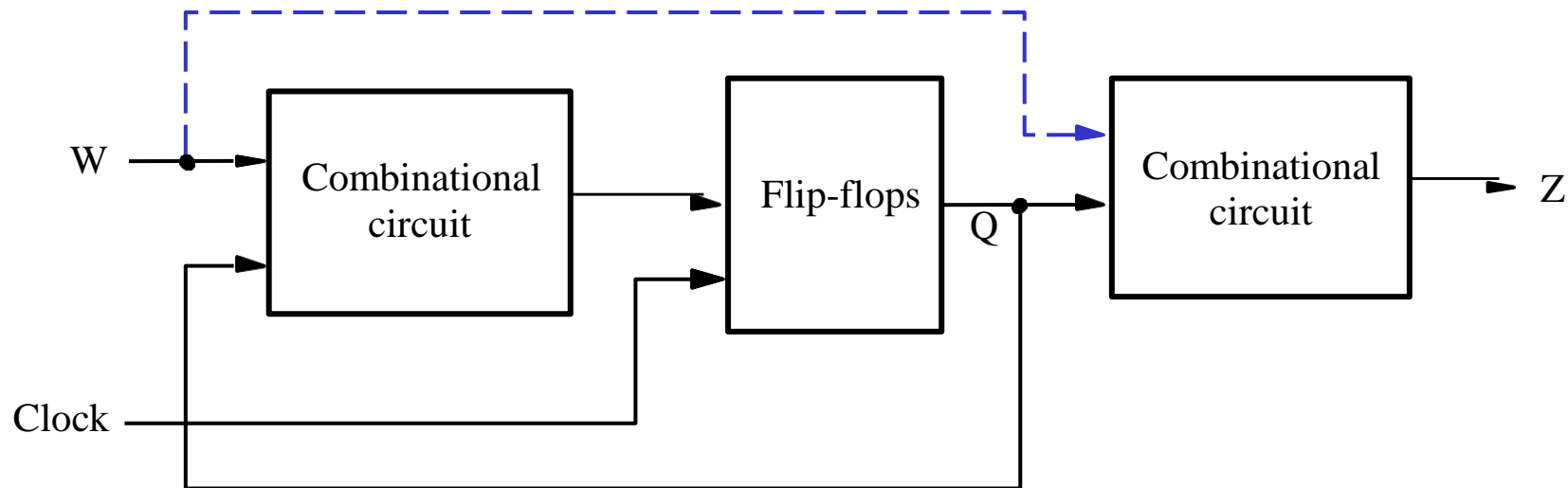

- The sequential circuits whose outputs depend only on the state of the circuit are of **Moore type**.
- Those whose outputs depend on both the state and the inputs are of **Mealy type**.

Moore State Model.

We wish to design such a circuit:


- The circuit has one input w and one output z .
- All changes in the circuit occur on the positive edge of a clock signal.
- The output z is 1 if during the past two clock cycles w was 1. Otherwise z is 0.

Clockcycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	0	1	0	0	1	1	0

Sequences of input and output signals.

Moore State Model.


Sequences of input and output signals.

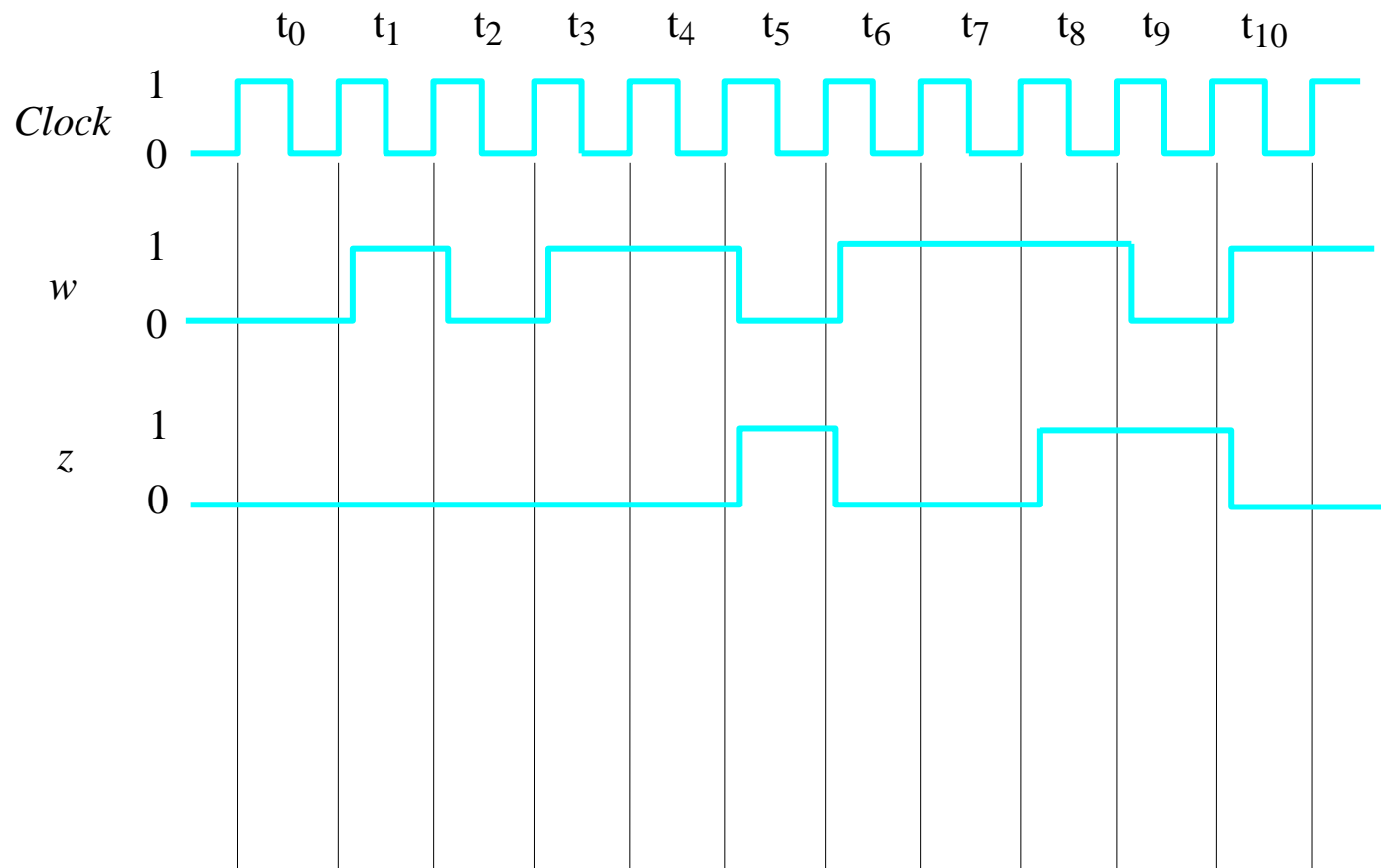

Moore State Model.

State Diagram

 - State A: w is 0 during past 1 clock cycle.
- State B: w has been 1 for just 1 clock cycle.
- State C: w has been 1 for 2 clock cycles.



Moore State Model.

State Table

Present state	Next state		Output z
	$w = 0$	$w = 1$	
A	A	B	0
B	A	C	0
C	A	C	1

	Present state	Next state		Output z
		$w = 0$	$w = 1$	
	y_2y_1	Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Moore State Model.

Next-State and Output Expressions

$w \backslash y_2 y_1$		00	01	11	10
		0	1	d	0
0	0	0	0	d	0
1	1	1	0	d	0

$$Y_1 = w y_1 \bar{y}_2$$

$y_2 \backslash y_1$		0	1
		0	0
0	0	0	0
1	1	1	d

$$z = y_2$$

$w \backslash y_2 y_1$		00	01	11	10
		0	1	d	0
0	0	0	0	d	0
1	0	0	1	d	1

$$\begin{aligned} Y_2 &= w y_1 + w y_2 \\ &= w (y_1 + y_2) \end{aligned}$$

Moore State Model.


Implementation

Output z depends on the state only.

1


	0	1
0	0	0
1	1	d

$$z = y_2$$

 

Moore State Model.

The timing diagram for that circuit

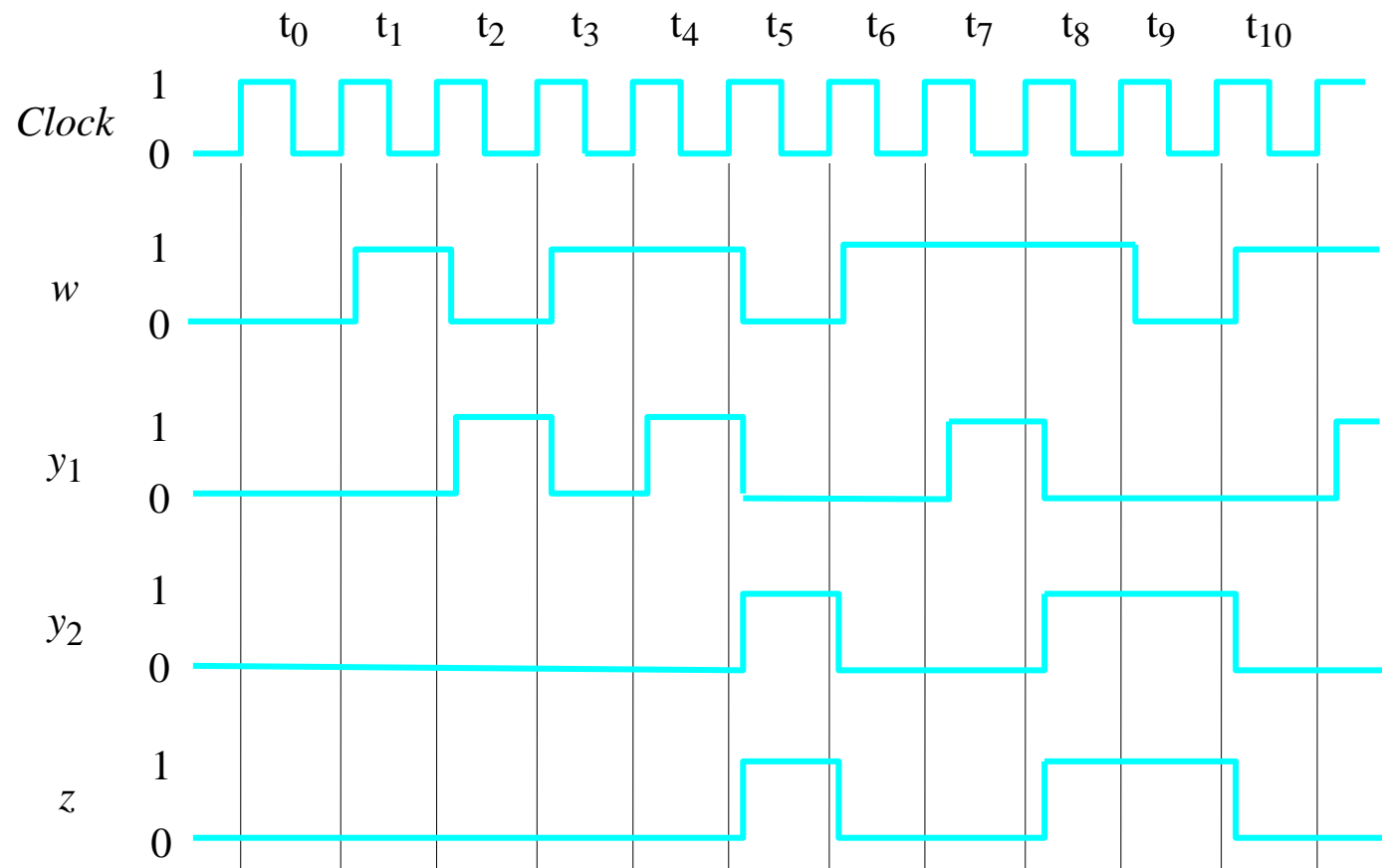

Moore State Model.

Alternative State Assignment

	Present state y_2y_1	Next state		Output z
		$w = 0$	$w = 1$	
		Y_2Y_1	Y_2Y_1	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

$$Y_1 = w$$

$$Y_2 = wy_1$$

$$z = y_2$$

Moore State Model.


Improved
Implementation

Timing diagram for
 z is the same but
those for y_1 and y_2
change.

$$Y_1 = w$$

$$Y_2 = wy_1$$

$$z = y_2$$

 

Mealy State Model.

We wish to design such a circuit:


- The circuit has one input w and one output z .
- The output z is 1 in the clock cycle when the second occurrence of $w = 1$ is detected. Otherwise z is 0.

Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Sequences of input and output signals.

Mealy State Model.


Sequences of input and output signals.

 

Mealy State Model.

State Diagram

 - State A: w is 0, producing an output $z = 0$.
- State B: w is 1.
- If $w = 1$ for two consecutive clock cycles, the machine remains in state B and produce an output $z = 1$.



Mealy State Model.

State Table

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1


	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Mealy State Model.

Implementation

$$Y = D = w$$


$$z = wy$$

 

Output z depends on both the state and the input.

Mealy State Model.

The timing diagram for that circuit

 


Verilog Code for the Moore FSM.

```
module simple (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output z;
  reg [2:1] y, Y;
  parameter [2:1] A = 2'b00, B = 2'b01, C =
2'b10;
```

```
  // Define the next state combinational
  circuit
```
 
```
    always @(w, y)
      case (y)
        A: if (w) Y = B;
           else Y = A;
        B: if (w) Y = C;
           else Y = A;
        C: if (w) Y = C;
           else Y = A;
        default: Y = 2'bxx;
      endcase
```




```
  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;
```

```
  // Define output
  assign z = (y == C);
```

```
endmodule
```

Verilog Code for the Moore FSM.

 

```

module simple (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output z;
  reg [2:1] y;
  parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10;

  // Define the sequential block
  always @(negedge Resetn, posedge Clock)
    if (Resetn == 0)      y <= A;
    else
      case (y)
        A: if (w) y <= B;
           else y <= A;
        B: if (w) y <= C;
           else y <= A;
        C: if (w) y <= C;
           else y <= A;
        default: y <= 2'bxx;
      endcase

  // Define output
  assign z = (y == C);


endmodule
  
```

Verilog Code for the Mealy FSM.

```
module mealy (Clock, Resetn, w, z);
  input Clock, Resetn, w;
  output reg z;
  reg y, Y;
  parameter A = 1'b0, B = 1'b1;
```

```
  always @(w, y)
    case (y)
```
 
```
      A: if (w)
          begin
              z = 0;
              Y = B;
          end
      else
          begin
              z = 0;
              Y = A;
          end
    endcase
```



```
      B: if (w)
          begin
              z = 1;
              Y = B;
          end
      else
          begin
              z = 0;
              Y = A;
          end
    endcase
```

```
  // Define the sequential block
  always @(negedge Resetn, posedge
Clock)
    if (Resetn == 0) y <= A;
    else y <= Y;


endmodule
```

Verilog Code for the FSM.

State Assignment

- State assignments are specified by a **parameter** statement in Verilog code.
- Verilog compilers can recognize the code for an FSM.
- They can optimize the implementation by looking for a better state assignment based on the cost of implementation.
- The user can either allow the compiler to optimize the state assignment or suppress it.

Verilog Code for the FSM.

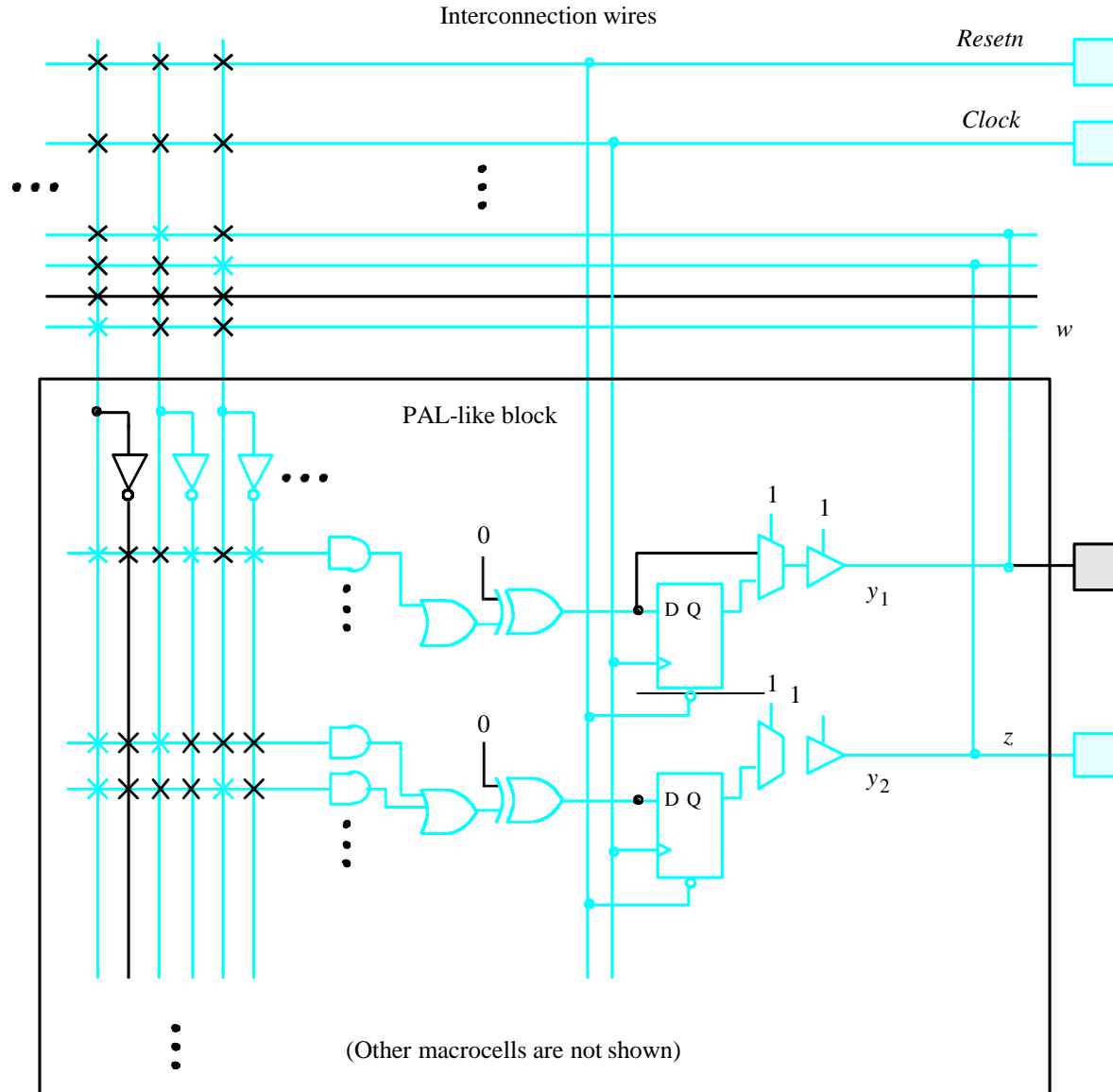

- The code for the Moore one is synthesised in a CPLD.
- The used parts are highlighted in blue.

$$Y_1 = wy_1 \bar{y}_2$$

$$\begin{aligned} Y_2 &= w y_1 + w y_2 \\ &= w (y_1 + y_2) \end{aligned}$$

$$z = y_2$$